

UNIT-1

B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

Ques. What do you mean by doping? Describe its need. Differentiate between n-type & p-type semiconductor.

Soln: Doping is the process of adding impurities to intrinsic semiconductor. Trivalent & pentavalent atoms are used for doping. When trivalent impurities are added then it becomes p-type semiconductor. When pentavalent impurities are added then it becomes n-type semiconductor.

Need of Doping: Doping is done to increase the conductivity of semiconductor devices. Doping creates extra holes or extra electrons to increase the flow of current. So conductivity of intrinsic semiconductor increases.

DIFFERENTIATE BETWEEN N-TYPE & P-TYPE SEMICONDUCTOR


N-Type	P-Type
1. Pentavalent impurities such as P, As, Sb are added.	1. Trivalent impurities such as Al, B, Ga are added.
2. Impurities are called donor atoms.	2. Impurities are called acceptor atoms.
3. Majority carriers are electrons & minority carriers are holes.	3. Majority carriers are holes & minority carriers are electrons.
4. The donor energy level is close to conduction band.	4. The acceptor energy level is close to valence band.

Ques 2. Discuss the formation of depletion layer in diode. Also explain the effect of temperature on diode.

Soln: When a p-n junction is formed then hole starts to move from p to n & electron starts to move from n to p due to concentration gradient. This is called Diffusion Process. An electric field is generated.

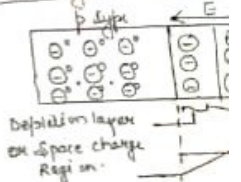B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

Ques 10. Define the term depletion layer or space charge region. What is its value of depletion layer or space charge region?



Effect of temperature on the p-n junction.

Forward Bias Condition: In this condition, the p-n junction is forward biased. The current increases exponentially with the voltage. The relationship is given by $I = I_s (e^{V/V_T} - 1)$.


Reverse Bias Condition: In this condition, the p-n junction is reverse biased. The current is very small and is called the reverse saturation current I_s . The relationship is given by $I = -I_s$.

Breakdown voltage (V_Z): The breakdown voltage is the voltage at which the reverse current increases rapidly. It is denoted by V_Z . The relationship is given by $I = -I_s$.

Ques 10. Define the term Full Wave Rectifier. What is its value of ripple factor?

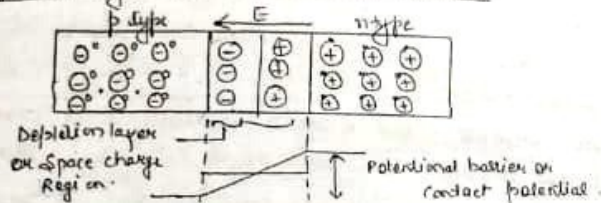B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]


at the junction, which stops the further movement of electrons & holes. So, a layer of immobile ions is formed at the junction. This layer is called depletion layer or SPACE CHARGE REGION.



Effect of temperature on the P-n junction diode -

- Forward Bias Condition:** In this case, the characteristics of diode shift to the left at a rate of $2.5 \text{ mV}/^\circ\text{C}$ rise in temperature & vice versa.
- Reverse Bias Condition:**
 - Reverse Current:** Reverse current increases with increase in temperature & vice versa. Let I_{S1} : Reverse current at temp. T_1 & vice versa. I_{S2} : Reverse current at temp. T_2 .

$$I_{S2} = I_{S1} \left[2 \frac{T_2 - T_1}{10} \right] = I_{S1} (2 \frac{\Delta T}{10})$$
 - Generally it doubles for every 10°C rise in temperature.
 - Breakdown voltage (V_Z):** Breakdown voltage increases with increase in temperature & vice versa.

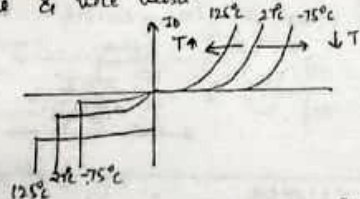

Ques 10. Define the term ripple factor. Derive the expression. What is its value of ripple factor for a Half Wave Rectifier & a Full Wave Rectifier?

B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

Sol: The output of rectifier has AC component (ripple) & DC component both. Ripple factor measures, how much amount of AC component is present in the output. So the effectiveness of a rectifier depends on the magnitude of ripple in the output. Smaller the ripple more effective is the rectifier. "Ripple factor is defined as the ratio of rms value of AC component to the DC component in the rectifier."

$$r = \frac{I_{ac}}{I_{dc}}, \text{ but } I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

dividing both sides with I_{dc}

$$\frac{I_{ac}}{I_{dc}} = \frac{1}{I_{dc}} \sqrt{I_{rms}^2 - I_{dc}^2} = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

for Half Wave rectifier: $I_{rms} = I_m/2$ $I_{dc} = I_m/\pi$

$$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\frac{\pi^2}{4} - 1}$$

$$r = 1.21$$

So ripple factor of Half wave rectifier is Very High.

for Full Wave rectifier [Center-Tapped Rectifier or Bridge Rectifier]

$$r = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1} \quad ; I_{rms} = I_m/\sqrt{2} \quad I_{dc} = 2I_m/\pi$$

$$r = \sqrt{\left(\frac{\pi}{\sqrt{2}}\right)^2 - 1}$$

$$r = \sqrt{\frac{\pi^2}{4} - 1} = 0.48$$

$$r = 0.48$$

Ques 12. In the bridge rectifier circuit, the secondary voltage $V_s = 100 \text{ sin } \omega t$ & load resistance is $1 \text{ k}\Omega$: (i) DC current (ii) RMS value of current (iii) Efficiency (iv) Ripple factor.

B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

Solⁿ: Given: $V_s = 100 \sin 50t$, $R_L = 1k\Omega$, $\beta = 0$
 $V_m = 100$
 $I_m = \frac{V_m}{R_L + \beta} = \frac{100}{1 \times 10^3 + 0} = 100mA$

$$I_{dc} = \frac{2 I_m}{\pi} = \frac{2 \times 100 \times 10^{-3}}{\pi} = 63.66 mA$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{100 \times 10^{-3}}{\sqrt{2}} = 70.7106 mA$$

$$\text{Efficiency} = \frac{\text{dc o/p power}}{\text{ac o/p power}}$$

$$\text{dc o/p power} = I_{dc}^2 \times R_L = \left(\frac{200}{\pi}\right)^2 \times 10^{-6} \times 1 \times 10^3 = 4.0528 W$$


$$\text{ac o/p power} = I_{rms}^2 (R_L + \beta) = \left(\frac{100}{\sqrt{2}}\right)^2 (1 \times 10^3) = 5.0 W$$

$$\text{Efficiency} = \frac{4.052}{5.0} \times 100 = 0.8104 \times 100 = 81.04\%$$

$$\text{Ripple factor } r = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1} = \sqrt{\left(\frac{70.7106}{63.66}\right)^2 - 1} = \sqrt{0.2332}$$

$$r = 0.48$$

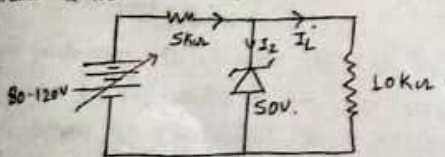Q13. For the circuit shown below, determine the value of maximum & minimum Zener diode current.



B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

Solⁿ: Zener diode act as the voltage regulator in the circuit & the voltage supply is variable hence, excess of voltage over 50V will across 5kΩ resistance.

Thus, minimum voltage across 5kΩ resistance is 80V-50V
 Current through 5kΩ resistance is $I_1 = \frac{30}{5000} = 6mA$

Also, maximum voltage across 5kΩ resistance is 120V-50V
 Current through 5kΩ resistance is $I_1' = \frac{70}{5000} = 14mA$

Now, voltage across load resistance of 10kΩ is 50V

Thus, current through 10kΩ will be $I_2 = \frac{50}{10000} = 5mA$

Hence, maximum current through Zener diode is

$$I_{Zmax} = I_1' - I_2 = 14 - 5 = 9mA$$


minimum current through zener diode is

$$I_{Zmin} = I_1 - I_2 = 6 - 5 = 1mA$$

$$I_{Zmax} = 9mA$$

$$I_{Zmin} = 1mA$$

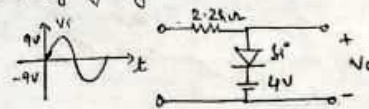Ques 14 Differentiate between clipper & clamper circuit. Determine draw output voltage for given network.



CLIPPER


1. Clipper limits the amplitude of the output voltage.
2. Output voltage is less than the input voltage.
3. Energy storage component is not required.

CLAMPER


1. Clamper shifts the DC level of the output voltage.
2. Output voltage is multiples of input voltage.
3. Energy storage component is required i.e. Capacitor is used.

B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

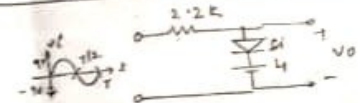
1. DC level remains same.
2. Shape of the output waveform changes.
3. Applications: Transmitters, Receivers, amplitude selector etc.
4. DC level remains same.
5. Shape of the output waveform changes.
6. Applications: Circuits, S.




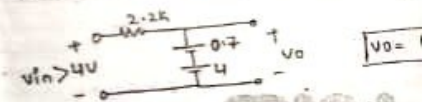
Case 1 0 to T/2 ; when $V_{in} > 4V$, $V_o = 1$



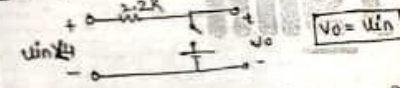$V_{in} < 4V$, Diode is Reverse Bias, hence $V_o = V_{in}$



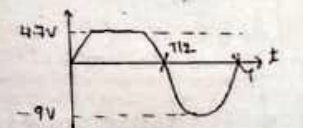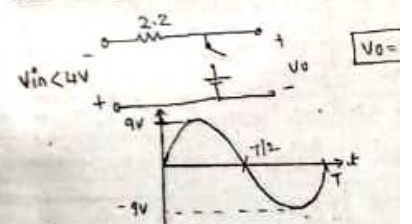Case 2 T/2 to T ; when $V_{in} < 4V$, $V_o = V_{in}$



as in the circuit & the voltage over 50V will be

distance is $80V - 50V = 30V$
 $\frac{30}{1000} = 6mA$

is $120V - 50V = 70V$
 $\frac{70}{5000} = 14mA$

is 50V
 $\frac{50}{10000} = 5mA$

is 14-5 = 9mA

is 6-5 = 1mA


circuit. Determine

ER

DC level of the multiples of input


moment is required

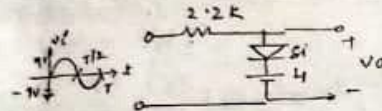4. DC level remains same.
 5. Shape of the Output waveform changes.
 6. Applications: Transmitters, receivers, amplitude selector etc.
4. DC level get shifted.
 5. Shape of the Output waveform remains same as input waveform.
 6. Applications: In Voltage multiplication circuits, Sonar, Radar system etc.




Stunt clipper -


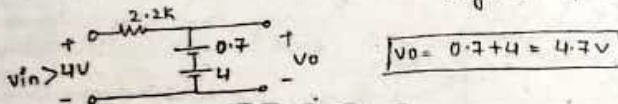
Case 1 $0 \leq t \leq T/2$; when $V_{in} > 4V$, Diode is forward Bias as for S_1 $V_p = 0.7V$



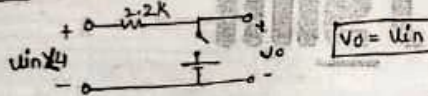
$V_{in} < 4V$, Diode is Reverse Bias, hence open switch.



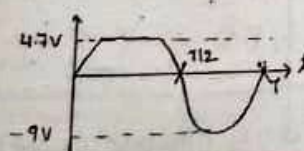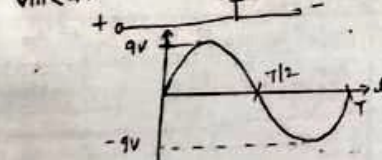Case 2 $T/2 \leq t \leq T$; when $V_{in} < 4V$, Diode will be Reverse Bias, hence open switch.




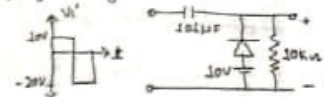Ques: Explain Positive & Negative clamper using suitable circuit diagram & input/output waveform. Determine output voltage for the given network.



Soln: Positive Clamper:

It shifts the ac signal in upward direction then clamper is called positive clamper.


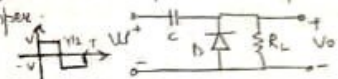


Case 1: $0 \leq t \leq T/2$; Diode is Reverse Bias Capacitor is charged to $-V_i$


$V_o = 2V$

Case 2: $T/2 \leq t \leq T$; Diode is Forward Bias capacitor is charged

$V_o = 0$

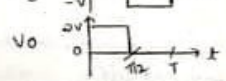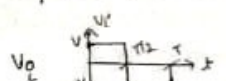

Negative clamper: It shifts the ac signal in downward direction then clamper is called Negative clamper.

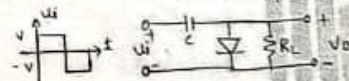

Case 1: $0 \leq t \leq T/2$; Diode is Forward Bias. Capacitor is charged to V_i


$V_o = 0$

Case 2: $T/2 \leq t \leq T$; Diode is Reverse Bias Capacitor is charged


$V_o = -2V$




Positive Clamper:

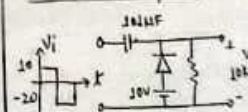

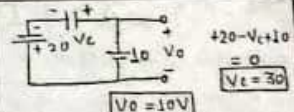Negative Cycle: $V_{in} = -20V$ Diode is ON & circuit is drawn.



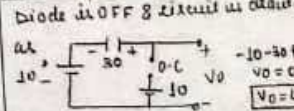Positive cycle: $V_{in} = 10V$ Diode is OFF & circuit is drawn



Q.3 Draw & explain the V-I characteristic of a P-N Junction diode. Also describe the effect of temperature on diode.

Sol: V-I characteristic of P-N Junction diode:-

diode current equation is:-

$$I_D = I_S [e^{V_D/\eta V_T} - 1] \quad \text{--- (1)}$$

where I_D = diode current

I_S = Reverse saturation current

V_D = diode voltage

V_T = volt equivalent of temperature

η = Ideality factor for $\eta = 1 \rightarrow \text{Ge}$

$\text{Si} \rightarrow \eta = 2$

$V_T = \frac{T}{11600}$ volt (T should be in kelvin) at room temp $V_T = 26 \text{ mV}$.

① Unbiased condition:- $V_D = 0$
 $I_D = I_S [e^{V_D/\eta V_T} - 1]$ where $V_D = 0$

then $I_D = I_S [e^{0/\eta V_T} - 1] = I_S [1 - 1]$

$$I_D = I_S [0] = 0 \quad \boxed{I_D = 0}$$

So curve passes through the origin.

② Forward bias condition:- $V_D = +ve$

$$I_D = I_S [e^{+V_D/\eta V_T} - 1]$$

$$\text{But } e^{V_D/\eta V_T} \gg 1$$

Therefore equation 1 becomes

$$I_D \approx I_S (e^{V_D/\eta V_T})$$

Hence forward characteristics is of exponential in nature.

③ Reverse bias:-

$$V_D = -ve$$


$$I_D = I_S [e^{-V_D/\eta V_T} - 1]$$

$$= I_S [\frac{1}{e^{V_D/\eta V_T}} - 1]$$

$$\text{But } \frac{1}{e^{V_D/\eta V_T}} \ll 1$$

So equation 1 becomes

$$I_D \approx -I_S$$

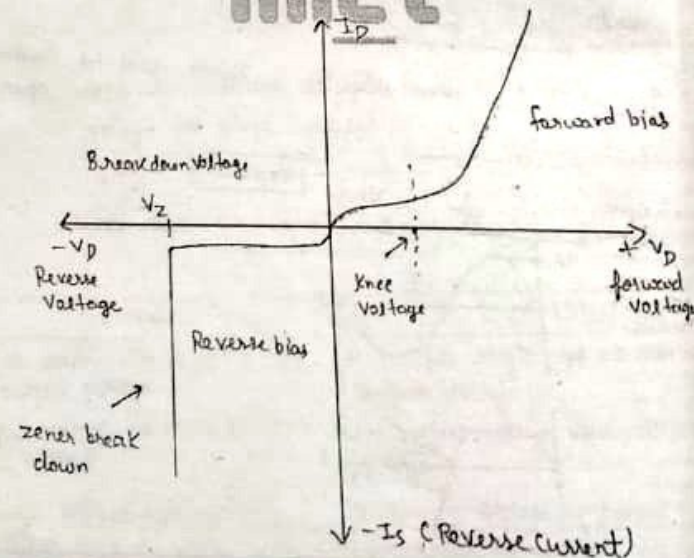

effect of temperature on

a) Forward bias:- In case of Si diode shift to the left with increase in temp. and vice-versa.

b) Reverse bias condition:- with increase in temp. at temp T_1 then at temp T_2

$$I_{S2} = I_{S1} [2^{T_2 - T_1}]$$

$$\boxed{I_{S2} = I_S}$$

④ Breakdown voltage (V_Z):- Breakdown voltage

Q.4 Explain the knee voltage. The Reverse saturation current is $10 \mu A$ at $300^\circ C$ applied to obtain the knee voltage.

Sol: knee voltage:- required to start this minimum or cut-off

for Ge

for Si


effect of temperature on V-I characteristic of P-N Junction diode:-
 (a) Forward bias:- In case of forward bias region the characteristic of Si diode shift to the left at a rate of $2.5 \text{ mV}/^\circ\text{C}$ rise in temp. and vice-versa.

(b) Reverse bias condition:- (i) Reverse current:- Reverse current increases with increase in temp. and vice versa. Let I_{S1} is the reverse current at temp T_1 then at temp T_2 , I_{S2} can be calculated as:-

$$I_{S2} = I_{S1} [2^{(T_2 - T_1)/10}] = I_{S1} [2^{\Delta T/10}]$$

$$I_{S2} = I_{S1} [2^{\frac{\Delta T}{10}}]$$

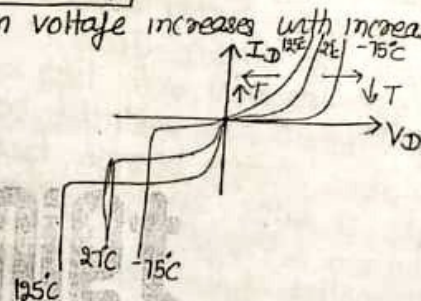(ii) Breakdown voltage (V_Z):- Breakdown voltage increases with increase in temp



Q.4 Explain the knee voltage. what is knee voltage of Ge, Si & P the Reverse saturation current of Si P-n Junction diode is $10 \mu\text{A}$ at 300K . determine the forward bias voltage to be applied to obtain diode current of 100 mA .

Sol: knee voltage:- A minimum positive voltage is required to start conduction in a forward biased diode. this minimum positive voltage is called knee voltage or cut-off voltage (V_r).

$$\text{For Ge } V_r = 0.3 \text{ V}$$

$$\text{For Si } V_r = 0.7 \text{ V}$$

Q.4 The reverse saturation current of Si P-n junction diode is $10 \mu\text{A}$ at 300K . determine the forward bias voltage to be applied to obtain diode current of 100 mA .

Ans

$$I_D = I_S [e^{V_D/nV_T} - 1]$$

$$100 \times 10^{-3} = 10 \times 10^{-6} [e^{V_D/2 \times 0.026} - 1]$$

$$10001 = e^{V_D/0.0518}$$

taking $\ln$ on both side

$$9.21 = \frac{V_D}{0.0518}$$

$$V_D = 0.47 \text{ V}$$


Q.5 Explain the V-I characteristics of ideal diode in forward bias & Reverse bias conditions. Give all the equivalent / approximation circuits of a diode.

Ans Ideal equivalent circuit

In ideal diode, $R_f = 0$, $V_r = 0$ and $I_S = 0$.


An ideal diode can be used as a perfect switch.

V-I characteristics-

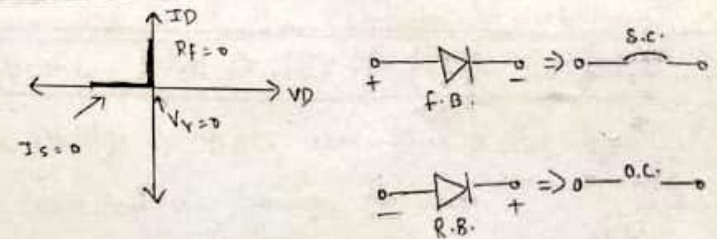


Equivalent circuits of a diode:-

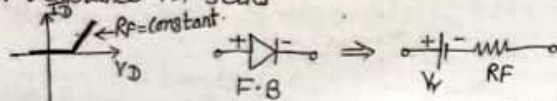
① Piecewise Linear equivalent circuits:- In this circuit diode can non linear characteristics is replaced by a straight line. So resistance of diode is constant. diode is replaced by battery with resistance in series.



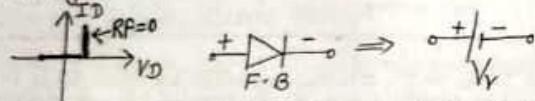② Simplified equivalent circuits:- Since diode forward resistance is low. So it can be neglected i.e. $R_F = 0$ diode is replaced by battery.



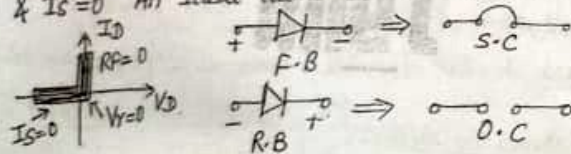③ Ideal equivalent circuit:- In ideal diode $R_F = 0$, $V_F = 0$ & $I_S = 0$. An Ideal diode can be used as a perfect switch.



Q.6) describe breakdown mechanism of diode. differentiate between avalanche and Zener breakdown.

sol: breakdown Mechanism:- If the reverse bias of P-N Junction is increased, a point will reach where the Junction breakdown & reverse current rises sharply. This specific value of the reverse bias voltage is called breakdown voltage (V_B). The following two process cause Junction breakdown.

① Zener breakdown:- It occurs in highly doped diode. In highly doped diode width of depletion layer is narrow. So electric field is very high. In depletion layer, so force is very high. This high force pulls valance electron into conduction band by breaking covalent bonds. These electrons become free electrons and will constitute a large reverse current. This is called Zener breakdown. Zener breakdown is negative i.e. raising the temp. will cause smaller break down voltage.

② Avalanche Breakdown:- It occurs in lightly doped diode. In lightly doped diode width of depletion layer is wide. So electric field and force are low. This low force can not break the covalent bond.

As reverse voltage is increased the kinetic energy ($\frac{1}{2}mv^2$) of minority carriers increases while travelling these minority carriers will collide with the stationary atom present in depletion layer & impart some of the kinetic energy to the valance electrons. These valance electrons will break their covalent bond and jump into conduction band to become free electrons.


Differentiate between avalanche and Zener breakdown.

S.N.	Zener Breakdown	Avalanche Breakdown
1.	Occurs in highly doped diode	Occurs in lightly doped diode
2.	The valance electrons are pulled into conduction band due to very high electric field	The valance electrons are pulled into conduction band due to impact of free electrons
3.	Tunneling effect occurs	Impact ionization occurs
4.	Occurs less than 6V	Occurs more than 6V
5.	Zener breakdown V-I characteristics is very sharp.	Avalanche breakdown V-I characteristics is not very sharp.
6.	Covalent bonds breaks directly.	Covalent bonds breaks indirectly.
7.	Temperature coefficient is negative.	Temperature coefficient is positive.

Differentiate between avalanche and zener breakdown.

S.N.	Zener Breakdown	Avalanche Breakdown
1.	Occurs in highly doped diode	Occurs in lightly doped diode.
2.	The valence electrons are pulled into conduction band due to very high electric field	The valence electrons are pushed into conduction band due to the energy imparted by collision of accelerated minority carrier.
3.	Tunneling effect occurs	Ionization effect occurs.
4.	Occurs less than 6V	Occurs greater than 6V.
5.	Zener breakdown V-I characteristics is very sharp.	It is not as sharp as that zener diode
6.	Covalent bonds break directly.	Covalent bonds break indirectly.
7.	Temperature coefficient is negative.	Temperature coefficient is positive.



Zener Diode Symbol

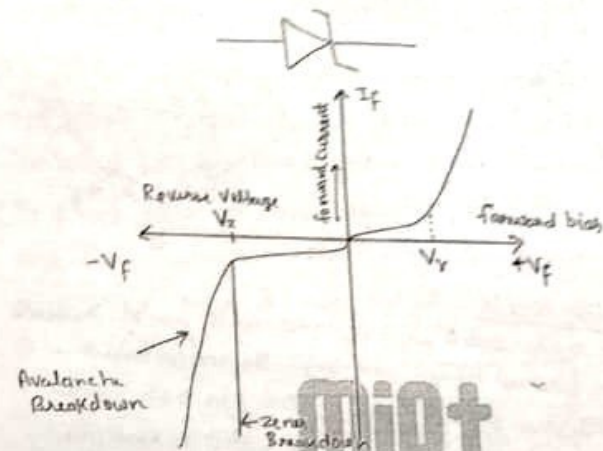

V-I characteristics of Zener Diode

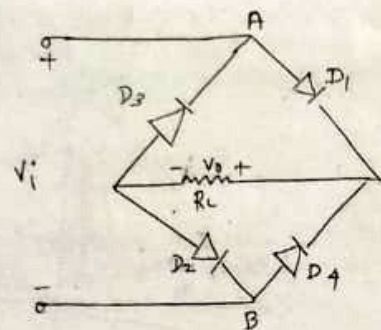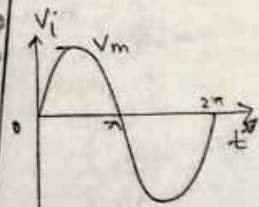Q.9 Explain the working of Bridge rectifier with diagram and derive the expression for rectification efficiency. What is PIV of Bridge Rectifier?



Ans- The bridge rectifier uses four diodes which are connected in bridge pattern.




Working-

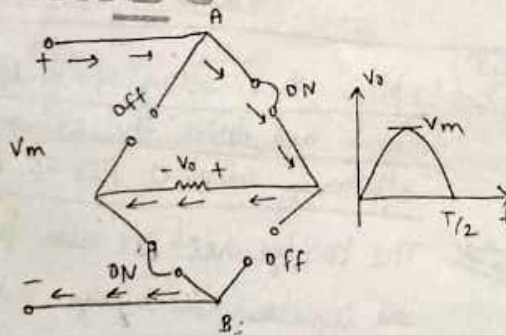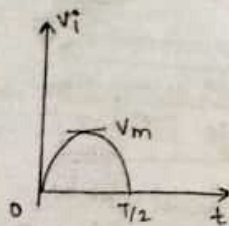(i) for positive cycle-


In positive cycle end A is +ve and end B is -ve. So diode D_1, D_2 are forward biased and D_3, D_4 are reverse biased. So, D_1, D_2 are ON and D_3, D_4 are OFF. Current flows through D_1, D_2 and give the output across load resistance.



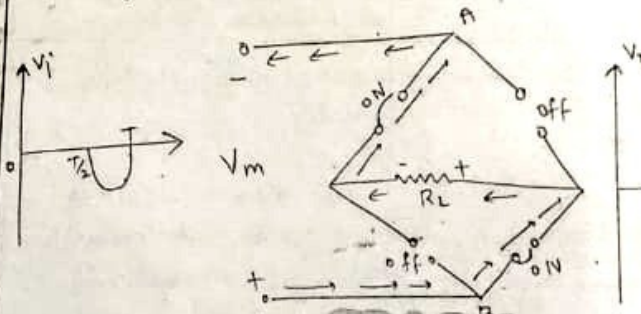ii) for negative cycle- In 'negative cycle' end A is negative and end B is positive. So diodes D_1, D_2 are reverse biased and D_3, D_4 are forward biased. So D_1, D_2 are off and D_3, D_4 are ON. Current flows through D_3, D_4 and give the output across load resistance R_L .



Input and output Waveform

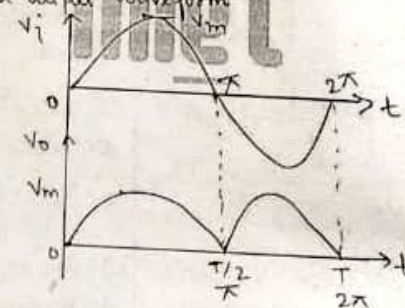

Rectification efficiency:-

$$\eta = \frac{\text{dc o/p Power}}{\text{ac i/p Power}} = \frac{P_{\text{dc}}}{P_{\text{ac}}}$$

$$= \frac{I_{\text{dc}}^2 \times R_L}{I_{\text{rms}}^2 \times (R_L + r_f)}$$

$$= \frac{\left(\frac{2I_m}{\pi}\right)^2 \times R_L}{\left(\frac{I_m}{\sqrt{2}}\right)^2 \times (R_L + r_f)}$$

if $r_f = 0$
 $\eta_{\text{max}} =$

PIV:- V_m

Compare half wave and

Parameter	Half wave rectifier	Center tap rectifier
Operation	Conducts during positive half cycles	Conducts both the cycles
V_{dc}	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$
V_{rms}	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$
Ripple factor	1.21	0.4
Efficiency	40.6%	81.2
PIV	V_m	$2V_m$
Ripple freq.	$f_r = f_i$	$f_r = 2f_i$

$$= \frac{\left(\frac{2I_m}{\pi}\right)^2 \times R_L}{\left(\frac{I_m}{\sqrt{2}}\right)^2 \times (R_L + r_f)}$$

$$\eta = \frac{0.812}{1 + \frac{r_f}{R_L}}$$

$$\text{if } r_f = 0$$

$$\eta_{\max} = 0.812 = 81.2\%$$

$$\text{PIV} = V_m$$



Q7 Compare half wave and full wave rectifier.

Ans-

S.N.	Parameter	Half wave rectifier	Centre tapped rectifier	Full wave Bridge Rectifier
1.	Operation	Conducts during positive half cycles.	Conducts during both the half cycles.	Conducts during both the half cycles.
2.	V _{dc}	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2V_m}{\pi}$
3.	V _{rms}	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$
4.	Ripple factor	1.21	0.48	0.48
5.	Efficiency	40.6%	81.2%	81.2%
6.	PIV	V _m	2V _m	V _m
7.	Ripple freq.	f _r = f _i	f _r = 2f _i	f _r = 2f _i

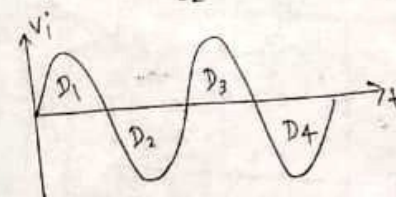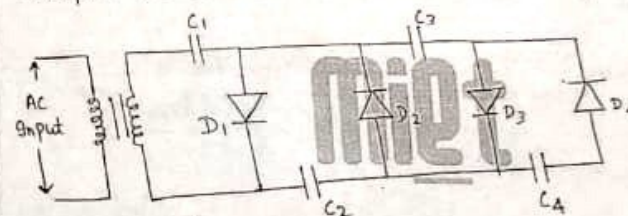Q.7 Explain the multiplier circuit half wave double, tripler, quadrupler. Define voltage Multiplier. Draw the circuit & explain working of voltage tripler & quadrupler circuit.

Ans- This circuit diagram is a general voltage multiplier circuit. It can perform function of voltage doubler, tripler, quadrupler. So for doubler two diodes and two capacitors are needed for tripler three diodes and three capacitors are needed. If we need nV_m at output we have to use n-diode & n capacitor.



Working- For the first positive cycle:- D₁ is ON. So capacitor C₁ charges up to voltage V_m.
V_{C1} = V_m

For first negative cycle:- D₂ is ON. So capacitor C₂ charges up to voltage 2V_m.

Applying KVL

$$V_m + V_{C2} - V_m = 0$$

$$V_{C2} = 2V_m$$

(iii) for second positive cycle:-

D_3 is ON. So capacitor C_3 charges upto voltage $2V_m$

Applying KVL

$$-V_m + 2V_m - V_{C3} + V_m = 0$$


$$V_{C3} = 2V_m$$

(iv) for second negative cycle:-

D_4 is ON. So capacitor C_4 charges upto voltage $2V_m$.

Applying KVL:- $-V_m - 2V_m + V_{C4} + 2V_m - V_m = 0$


$$V_{C4} = 2V_m$$

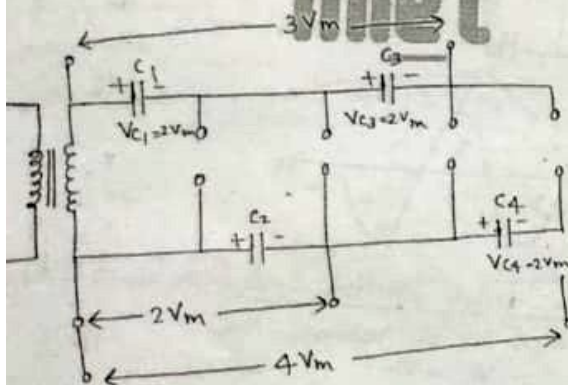


Q.8 Explain the working of full wave voltage doubler with help of a neat diagram or explain the working of a voltage doubler circuit.

Ans-


Voltage doubler:-

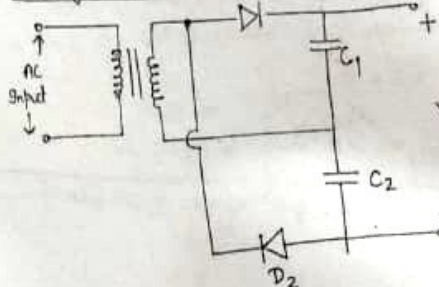

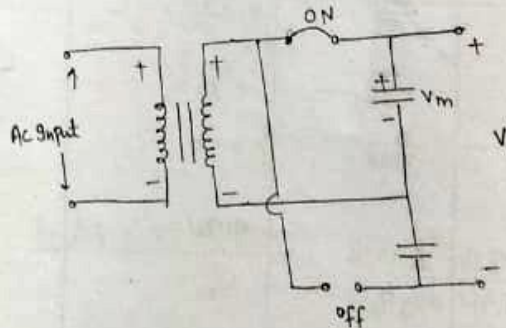Working- (i) for positive cycle- In positive cycle D_1 is forward biased but D_2 is reverse biased. So capacitor C_1 charges upto voltage V_m .




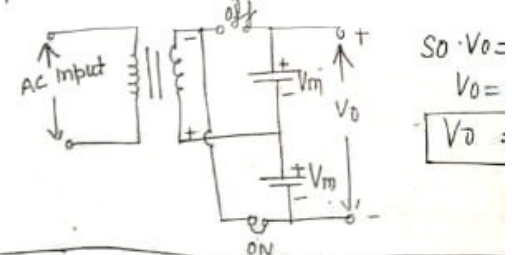For negative cycle:- In negative cycle D_2 is forward biased but D_1 is reverse biased. So capacitor C_2 charges upto voltage V_m .



So $V_o = V_m + V_m = 2V_m$

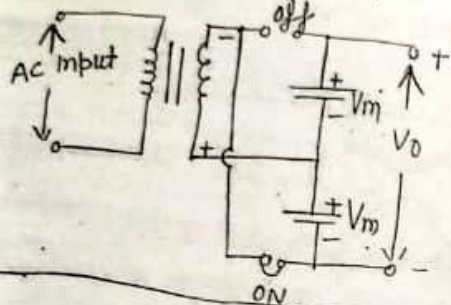Q1) For negative cycle:- In negative cycle D_1 is reverse biased but D_2 is forward biased. So capacitor C_2 charges up to voltage V_m .




$$So, V_o = V_{C1} + V_{C2}$$

$$V_o = V_m + V_m$$



$$V_o = 2V_m$$

miat

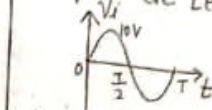Q11) Why bridge type full wave rectifier is preferred over centre tapped Full wave Rectifier. State two reasons. determine output waveform for the given N/w below. Also determine the output dc level and compute PIV of each diode.



Sol. for +ve cycle

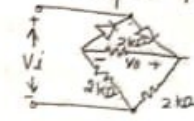
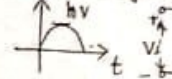


$$V_o = \frac{1}{2} V_i \text{ or } \frac{1}{2} V_{imax}$$

$$V_o = \frac{1}{2} \times 10$$

$$V_o = 5V$$


For -ve cycle:-

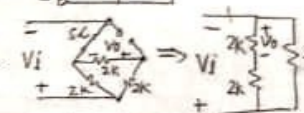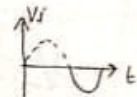

$$V_o = \frac{1}{2} V_i = \frac{1}{2} V_{imax}$$

$$V_o = \frac{1}{2} \times 10 = 5V$$


So o/p waveform:-

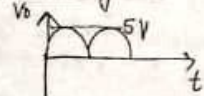

$$V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 5}{\pi} = 3.18$$

$$PIV = 5V$$


Centre tapped Full wave Rectifier:-

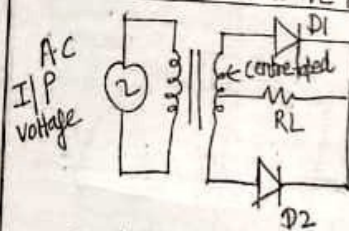


Centre tapped Rectifier have a centre tapped stepdown transformer. Two diode D_1, D_2 & Load resistance R_L . In centre tapped transformer secondary winding is

divided into two equal halves.

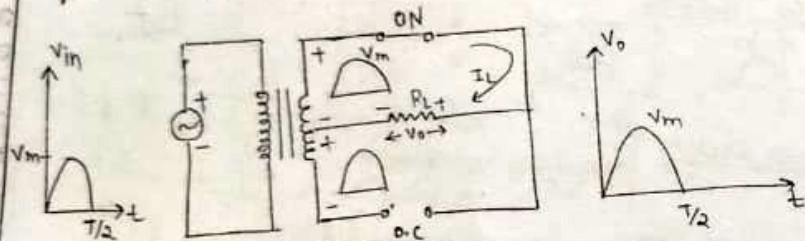
Working- (i) for positive half cycle, in positive half cycle diode D_1 is forward biased and D_2 is reverse biased. So D_1 is ON and D_2 is reverse biased OFF. Current flows through the upper half of secondary winding.



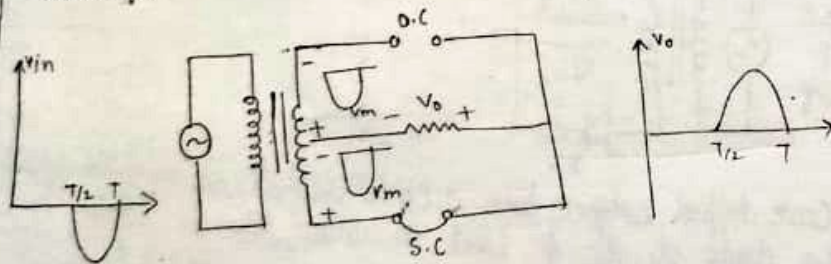(ii) for negative cycle - In negative cycle diode D_1 is reverse biased and diode D_2 is forward biased. So D_1 is off and D_2 is ON. Current flows through the lower half of secondary windings.



Input and output wave of rectifier-

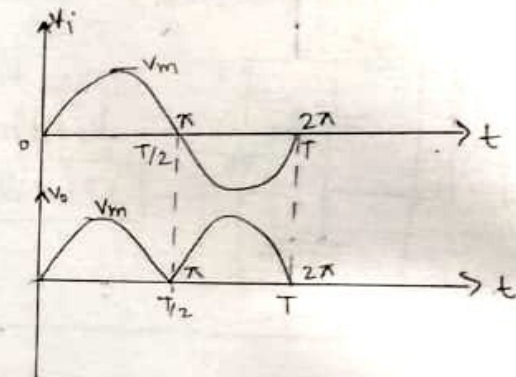


Q16 Explain Working and characteristic of diode & LED with the help of neat diagrams.

(a) Tunnel Diode

(b) LED

Ans- Tunnel Diode:-

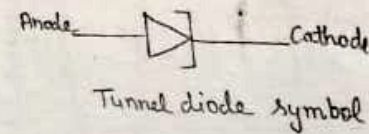

Tunnel diode symbol

- Tunnel diode is very highly doped diode.
- The doping of tunnel diode is 1000 times greater than simple diode.
- So, depletion layer is very narrow and is of the order of 10 nm.

Working of tunnel

Unbiased tunnel of n-type over

Small voltage

than a simple tunnel to

Applied voltage

increased.

exactly as

Applied voltage

of conduct

Applied voltage

band and

operate in

I_V

I_V

V

Working of tunnel diode-


(i) Unbiased tunnel diode- Due to high doping the conduction band of n-type overlaps with the valence band of p-type material.

(ii) Small Voltage is applied- When a small Voltage is applied, then a small number of electrons from conduction band tunnel to the valence band.

(iii) Applied Voltage is slightly increased- When voltage applied is increased, the energy level of n side conduction band becomes exactly equal to the energy level of p-side valence band.

(iv) Applied Voltage is further increased- A slight misalignment of conduction band and valence band takes place.

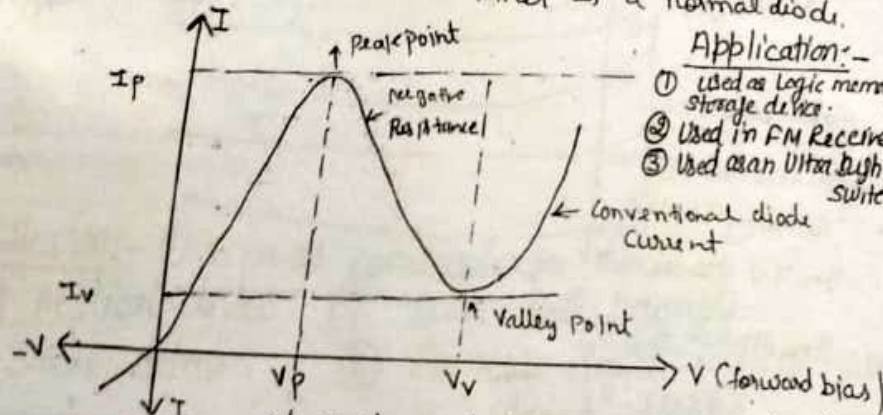(v) Applied Voltage is largely increased- At this point the conduction band and valence band no longer overlap and tunnel diode operate in the same manner as a normal diode.



Application:-

- ① Used as logic memory storage device.
- ② Used in FM Receiver
- ③ Used as an Ultra high speed switch



V-I characteristics of tunnel diode

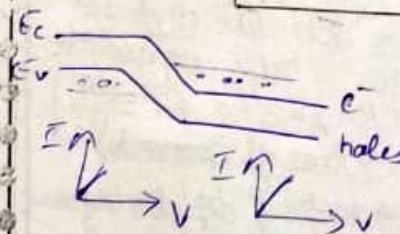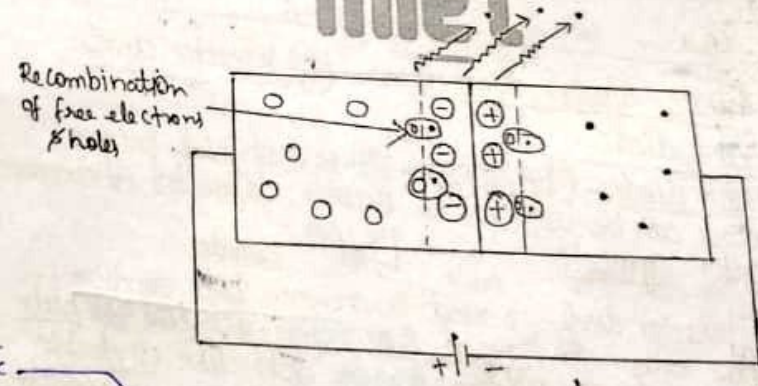(b) LED- Light Emitting diode (LED) is a photo electronic device which converts electrical energy into light energy. Material like gallium, phosphorus and arsenic are used for the manufacturing of LED.




Symbol

Working- When LED is forward biased then hole in p-type and electron in n-type start to cross the junction and recombine with each other. Simple diode (Ge, Si) produce heat in recombination.



V-I characteristics:-

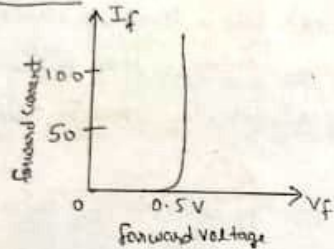


Application:-

- 1) Used in digital clocks
- 2) used in calculators.
- 3) used in mobile TV displays
- 4) used in seven segment displays.


Q.17 Write short Note on:- (a) Varactor diode

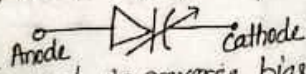(b) Photodiode

Sol: Varactor diode:- (VARICAP):- It is a special purpose diode which can be used as a variable capacitor in microwave circuit. Symbol:-




Working:- Varactor diode is used in reverse bias condition. In reverse bias, the P region & N region act like the plate of capacitor, while the depletion region acts like dielectric. So there exists a capacitance space charge capacitance or depletion region capacitance. It is given by $C_T = \frac{\epsilon A}{W}$
 $\epsilon \rightarrow$ permittivity of semiconductor
 $A \rightarrow$ Area of cross section
 $W \rightarrow$ width of depletion region.

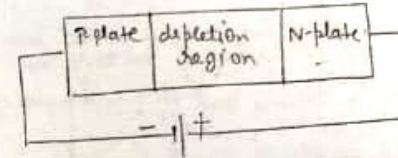

→ As the reverse bias applied to the diode increases, width of depletion region (W) increases. So, C_T decreases and vice-versa. Therefore capacitance controlled by applied voltage.


Characteristics:-

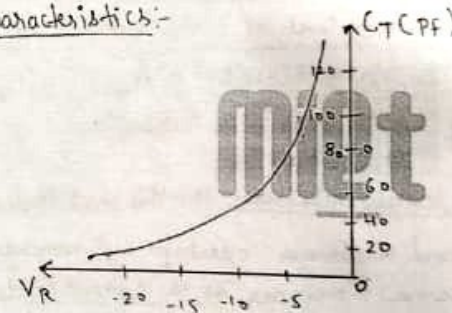

Application:-

- FM modulator
- Tuning circuit
- In TV receiver
- In radio receiver

Photo diode:- A photodiode is a semiconductor device that converts light into an electrical current.

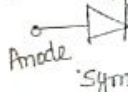

When a light falls on the junction, it creates electron-hole pairs. The electric field in the depletion region moves the electrons towards the cathode and holes towards the anode, creating a current. This is the photoelectric effect.


dark current

Application:-

- 1) Medical
- 2) Smoke


B. Tech I Year [Subject Name: Fundamentals Of Electronics Engineering]

Photo diode:- A photo diode is a semiconductor P-N Junction device that converts light into an electric current.

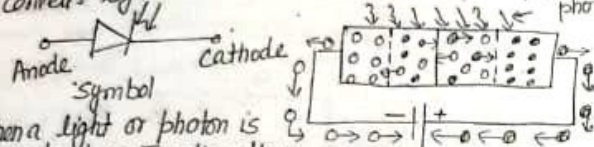

Working:- when a light or photon is used to illuminate P-n Junction then photon hits the immobile ions present in the depletion layer.
 ⇒ If energy of photon is greater than 1.1 eV than covalent bond will break. So electron hole pairs are generated.
 ⇒ Due to electric field electron hole pairs move away from the junction. Hence holes move to anode & electrons move to the cathode to produce photo current. This entire process is known as photo-electric effect.

V-I characteristic of photo diode:-

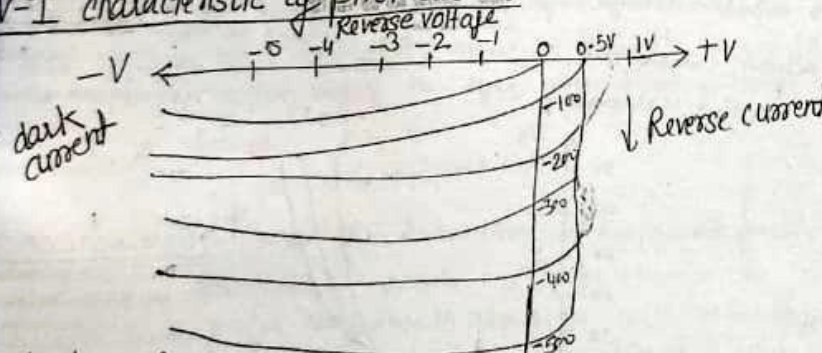


Application:- ① optical communication
 ② Medical device ③ solar cell pannels
 ④ Smoke detectors ⑤ Camera light meters and street lights.

1.1 eV

UNIT-2

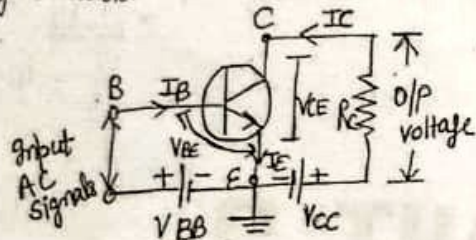Q.1) Describe the construction and working of a NPN transistor in CE configuration w.r. to size and doping. Also draw the input output characteristic graph.

Sol: CE (Common Emitter Configuration) :- In CE configuration input is applied b/w base and emitter while output is taken out from collector and emitter. So emitter of transistor is common to both input and output.



① DC current gain (β):-

It is the ratio of o/p current (I_C) to the input current (I_B).

$$\beta = \frac{I_C}{I_B}$$

Since value of $I_B \ll I_C$ so $\beta \gg 1$.
So current gain is available in CE Configuration.
Value of β varies from 20 to 500.

② Expression for output current:- $I_C = \alpha I_E + I_{CBO}$

$$I_C = \alpha (I_C + I_B) + I_{CBO} \quad (I_E = I_C + I_B)$$

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \left(\frac{\alpha}{1 - \alpha}\right) I_B + \left(\frac{1}{1 - \alpha}\right) I_{CBO} \quad \text{--- ①}$$

$$\text{but } \beta = \frac{\alpha}{1 - \alpha} \Rightarrow \frac{\alpha}{1 - \alpha} + 1 = \beta + 1$$

$$\frac{1}{1 - \alpha} = \beta + 1 \quad \frac{1}{1 - \alpha} = \beta + 1 \quad \text{--- ② using ① \& ②}$$


$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$I_C = \beta I_B + I_{CEO}$$

where I_{CEO} : leakage current b/w collector & emitter while base is open i.e. $I_B = 0$ $I_{CEO} = (\beta + 1) I_{CBO}$

Q.1 Draw the input and output characteristics of common emitter configuration.:-


Ans:-

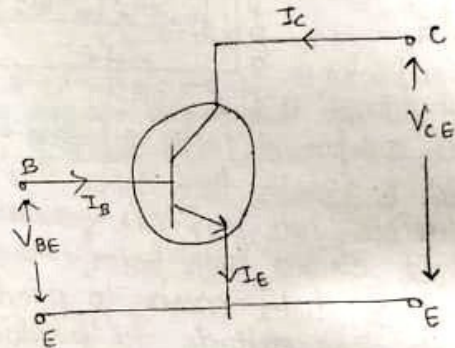

Input characteristics:- It is the graph between

input voltage for a constant output voltage. In

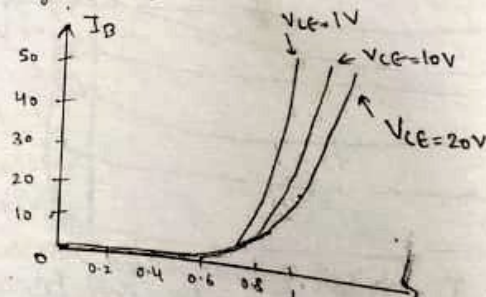input current is I_B and input voltage is V_{BE} while output voltage is V_{CE} .



input characteristics is identical to the V-I characteristics of forward biased p-n junction diode.

output characteristics-

Current and output for CBE output V_{CE} while input I_B

Saturation region

Active Region


I_{CBO} , which is max so graph of ac in I_C on char

Saturation region

active region to collector current cutoff region- When

small collector C in CE configura

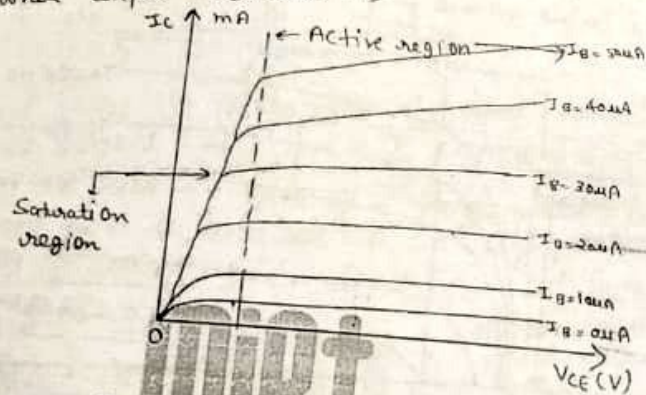Output characteristics- It is a graph between output current and output voltage for constant input current. For CBE output current is I_C and output voltage is V_{CE} while input current is I_B .



Active Region- For given β and I_B , I_C is dependent on I_{CBO} , which is more dependent on V_{CE} than the case in CB. So graph of active region has some slope showing change in I_C on changing in V_{CE} .

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

Saturation region- When the transistor is switched from active region to saturation region a large change in collector current for very small change in collector voltage.

Cutoff region- When both junction are reverse biased a very small collector current is obtained which is close to horizontal axis.

In CE Configuration $I_C = \beta I_B + (\beta + 1) I_{CBO}$.

Q2 Define α and β with respect to BJT and derive the relationship between them. A transistor having $\alpha = 0.975$ and reverse saturation current $I_{CBO} = 10 \mu A$ is operated in CE Mode. If the base current is $250 \mu A$, calculate I_E and I_C .

Sol: α :- It is the ratio of output current (I_C) to the input current (I_E). $\alpha = \frac{I_C}{I_E}$ Since $I_E > I_C$ so value of α is less than 1. Value of α ranges from 0.90 to 0.99. No current available in CB configuration.

β :- It is the ratio of output current (I_C) to the input current (I_B). $\beta = \frac{I_C}{I_B}$ value of $I_B \ll I_C$ so $\beta \gg 1$ and current is I_B available in CE configuration. Value of β varies from 20 to 500.

γ :- It is the ratio of O/P current (I_E) to the Input current (I_B). $\gamma = \frac{I_E}{I_B}$ Since value of $I_B \ll I_E$ so $\gamma \gg 1$ therefore current gain available in CC configuration. $\alpha = 0.975$ $I_B = 250 \mu A$ $I_{CBO} = I_{CEO} = 10 \mu A$

Numericals:-

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.975}{1 - 0.975} = \frac{0.975}{0.025} = 39$$

$$\boxed{\beta = 39}$$

Now for CE:- $I_C = \beta I_B + I_{CEO}$
 $I_C = 39 \times 250 \times 10^{-6} + 10 \times 10^{-6}$
 $I_C = 9.76 \text{ mA}$


$$I_E = I_C + I_B$$

$$I_E = 9.76 + 0.25$$


$$\boxed{I_E = 10.01 \text{ mA}}$$

Q3) Draw the input and output characteristics of common base (CB) configuration. Also write an expression for output current.

Ans

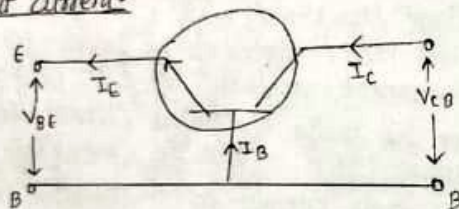

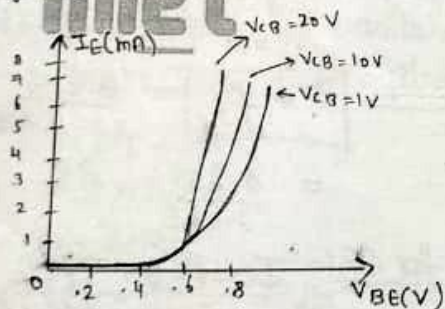
Input characteristics:- It is the graph between input current and input voltage for a constant output voltage. In CB configuration input current is I_E and input voltage is V_{BE} while output voltage is V_{CB} .



Important point

- Input characteristics is identical to the V-I characteristics of forward biased diode.
- As V_{CB} increases I_E increases slightly due to early effect.

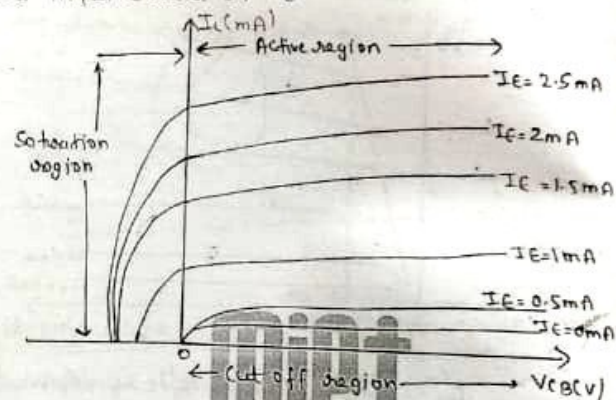Output characteristics:- It is the graph between output current and output voltage for constant input current. Common base output current is I_C and output voltage is V_{CB} while input current is I_E .




Active region:- for given α and I_E , I_C is dependent on I_{CBO} which is slightly depend on V_{CB} . So graph in active region is almost constant.

Saturation region:- When the transistor is switched from active to saturation region, a large change in electron current for very small value of forward bias voltage at collector to base junction is obtained in negative direction.

Cut-off region:- When both the junction are reverse biased a very small collector current is obtained. In CB configuration $I_C = \alpha I_E + I_{CBO}$.

Expression for Output

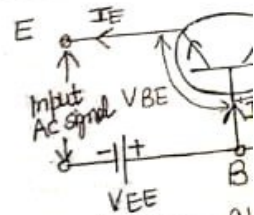

DC current gain:- It is the ratio of output current to input current. In CB configuration, the value of α is less than 1, so no current gain is obtained. Expression for α is given by:

then $I_C = I_E$ for CB. $I_C = I_E$ (Reverse Leakage Current) emitter is open.

Q4) what is Base Width?

Ans. Base Width is the width of the base layer. Forward bias profile is shown. The depletion layer is formed at the junctions, which is non-uniform. At the edges, the depletion layer is small. On the other hand, in the center, it is large.

output current
Common Base
voltage is V_{CB}

$I_E = 2.5 \text{ mA}$

$I_C = 2 \text{ mA}$

$I_E = 1.5 \text{ mA}$

$I_E = 1 \text{ mA}$

$I_E = 0.5 \text{ mA}$

$I_E = 0 \text{ mA}$

V_{CB}

dependent only
graph of

d from

electron


voltage

positive direct

biased

re-06

Expression for Output current:-

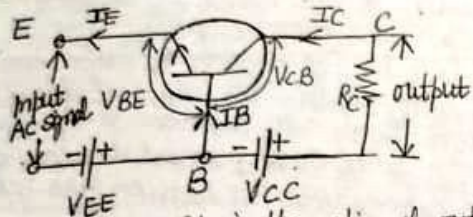


DC current gain:- It is the ratio of output current (I_C) to the input current (I_E). $\alpha = \frac{I_C}{I_E}$ since $I_E > I_C$ so value of α is less than 1. Value of α ranges from .90 to .99 so no current gain is available in CB configuration.

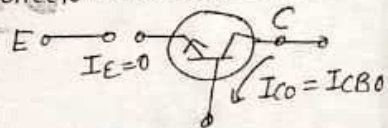ii) Expression for op current:- $I_C = I_{EC} + I_{CO}$ but $I_{EC} = \alpha I_E$ then $I_C = \alpha I_E + I_{CO}$ Collector current when emitter is open.

for CB $I_C = I_{CB0}$

(Reverse Leakage current b/w collector and base while emitter is open i.e. $I_E = 0$)




Q4) what is Base Width Modulation? How a transistor can be defined as a current operated device?

Ans Base Width Modulation:- In active region J_{EB} is forward bias and J_{CB} is reverse bias. Also doping profile is $D_E > D_C > D_B$. So width of depletion layer formed on E-B Junction and C-B Junction is non uniform. At J_{EB} major width of depletion is towards the base, so effective width of base is very small. On increasing V_{EB} effective width of base

base region further reduces. this effect is called base width modulation or early effect.

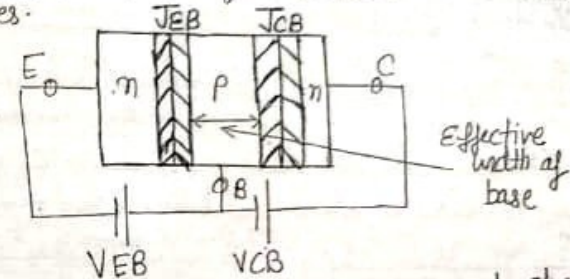On increasing V_{CE} I_E and I_C increases but I_B decreases (due to reduction in base width, possibility of recombination in this region reduces. thus α , β , γ increases.






transistor can be defined as a current operated device:-

BJT is called current controlled device. because output is controlled by input current. In BJT the base current controls the current flow from emitter to collector.

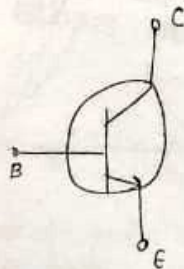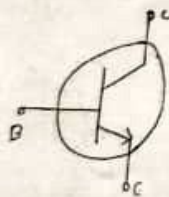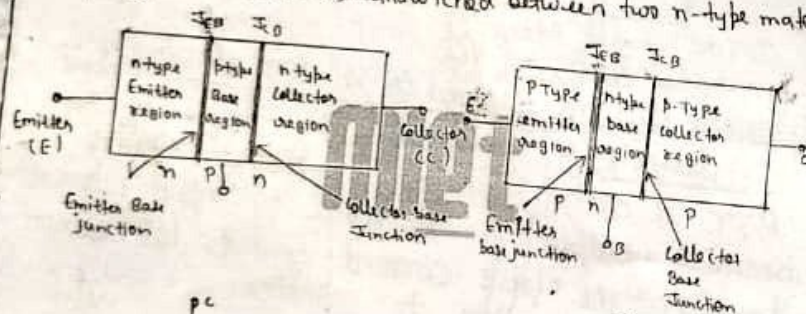Q.5
Q.5 Discuss the construction, doping profile and physical appearance of emitter base and collector of transistor.

Ans- Construction of transistor-

BJT consist of a layer of n type material sandwiched between two p-type materials or one p-type material is sandwiched between two n-type materials.



Symbol

Emitter:- It is the highest doping region in the transistor. It supplies (emits) carrier to the base. It supplies electrons to the base in npn and holes in pnp.

Base:- It is the middle part of transistor is called, very thin and lightly doped. So most of the carriers coming from emitter pass to collector.

Collector:- Collector collects the carriers which are coming from the base. Doping of collector is heavier than base but less than emitter.

Area profile :- $C > E > B$

doping profile :- $E > C > B$

B. Tech I
Why JFET is
Explain the

JFET. Draw
N/P channel
Construction

both side
two p-n j
connected b
are drain a
n/c contact p-dr



n-channel


operation:-

- When V_{gs} is from source layer at V_{ps} is layer just below

Why JFET is called voltage controlled device? Draw its structure & explain the construction and working of N channel JFET.

Draw the drain characteristics/output characteristic of N channel JFET indicate different regions and its significance?

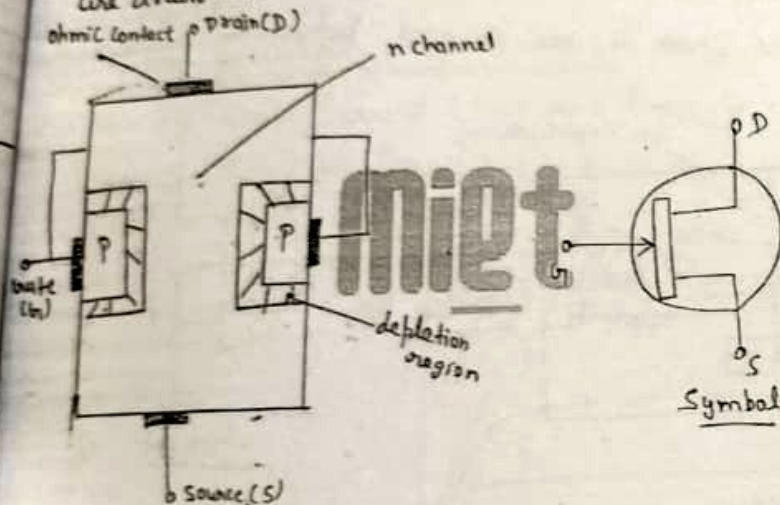Construction - A n channel JFET have n type base on both side of base two heavily doped p regions are formed. So two p-n junction are formed which are internally connected by a gate terminal and other two terminals are drain and source.



N-channel JFET

operation:- (i) V_{DS} = positive (>0) and $V_{GS}=0$

• When V_{DS} is increased more and more electrons move from source to drain. So current increases and depletion layer also increases. So, channel becomes narrower.

• If V_{DS} is further increased a condition comes when depletion layer just touches each other. This condition is called pinch-off condition.

• The value of V_{DS} which establish this condition is called pinch-off voltage (V_p). After pinch-off current becomes constant.

(ii) $V_{DS} = +ve (>0)$ and $V_{GS} = -ve (<0)$


- As V_{GS} is increased pinch off condition comes earlier and pinch-off voltage decreases in parabolic manner.
- At $V_{GS} = V_p$, current I_D will be zero.

JFET Characteristics

JFET has two types of characteristics

- Drain or output characteristics
- Transfer characteristics.

(i) Drain or Output characteristics:-

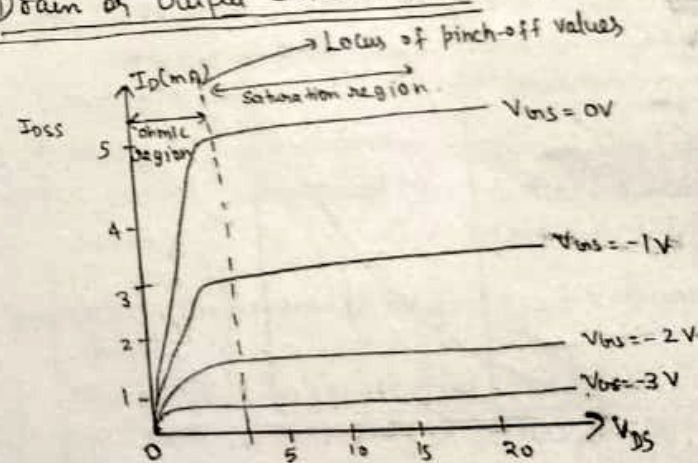


• ohmic region - The current I_D increases linearly with V_{DS} in ohmic region the slope of graph is dependent on V_{GS} . So FET can be used as voltage controlled resistance.

Saturation region or Active region -

→ After pinch-off condition the drain current (I_{DSS}) and this region is called saturation region. In this region JFET works as amplifier.

Transfer characteristics - It is the graph between drain current (I_D) and gate to source voltage (V_{GS}) while drain to source voltage (V_{DS}) should be constant. I_D & V_{GS} are related by Schokley eqn.

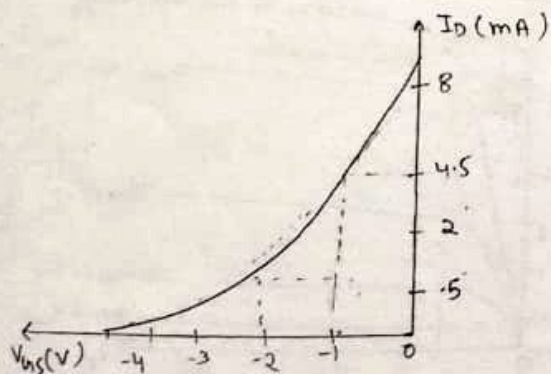
$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$



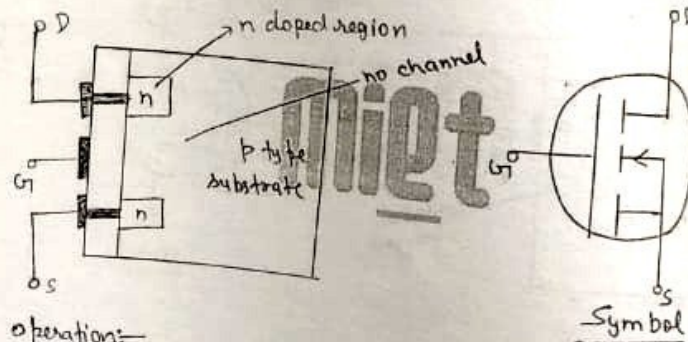Q3

Describe the construction working of MOSFET. Draw drain & Transfer characteristics.

Ans - Construction - N channel enhancement MOSFET. P type substrate. In p type substrate two n regions are formed. A thin layer of SiO_2 is deposited and source and drain are connected with the help of metal contact. There is no channel between two n regions.



operation -

- ci) $V_{DS} = +ve (> 0)$ and $V_{GS} = 0$
 • If V_{DS} is increased then no current will flow because there is no channel, i.e. $I_D = 0$
- cii) $V_{DS} = +ve (> 0)$ and $V_{GS} = +ve (> 0)$
 • If positive gate voltage is applied at gate then electrons in p type move towards the gate and hole move away from the gate.

Tile 2V no channel is formed.

This 2V is called threshold voltage. V_{GS} is further increased. This is called saturation region.

characteristics - It has two characteristics.

- 1) Drain or output characteristics - between drain current (I_D) and drain to source voltage (V_{DS}) at constant V_{GS} .

N/P
of enhancement
characteristics.

ent MOSFET.
two regions
drifted. Drain
metallic
regions.

DD

flow


gate
holes

4


- Till 2V no channel is formed. But after 2V channel is formed.
- This 2V is called threshold Voltage (V_t). If V_{gs} is further increased then I_D continuously increases. This is called enhancement MOSFET.

Characteristics - It has two types of characteristics.

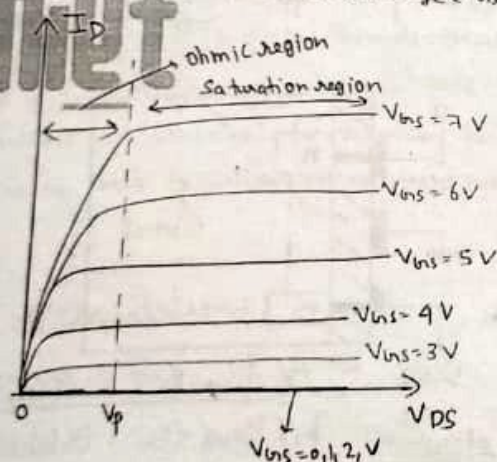c1) Drain or Output characteristics - It is the curve between drain current (I_D) and drain to source voltage (V_{DS}) at constant gate to source voltage (V_{gs}).



c11) Transfer characteristics :-

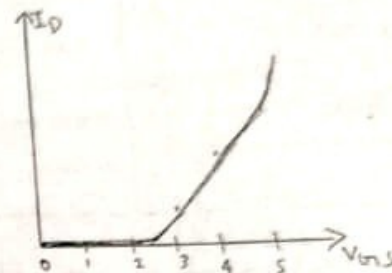

It is the curve between drain current (I_D) and gate to source voltage (V_{gs}) at constant drain to source voltage.

7
997

List the difference between JFET & BJT.
Define Pinch off voltage & transconductance (g_m)?

Ans-

	JFET	BJT
1.	It is unipolar device. i.e. operation depends only on majority carriers.	It is bipolar device i.e. operation depends on majority and minority carriers.
2.	Voltage Controlled device i.e. output is controlled by voltage.	Current Controlled device. i.e. output is controlled by current.
3.	Input impedance is very high.	Input impedance is very low.
4.	Temperature independent due to absence of minority carriers.	Temperature dependent due to presence of minority carriers.


Ques Explain the construction and working of n channel depletion type MOSFET. Also draw its drain and transfer characteristics.

Ans Construction - n channel depletion type MOSFET. Then two n regions are

connected with metallic contact. A n channel is formed between two n regions. Gate is insulated from n by SiO_2 . So I_b is zero. g-i is also called induced gate field effect transistor (IGFET)

Substrate

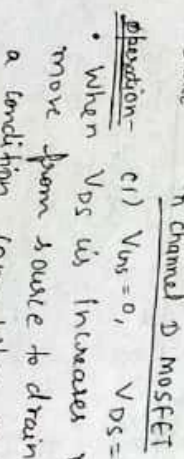
n channel D MOSFET
 (c) $V_{GS} = 0$, $V_{DS} =$



This condition is C
of Vos which establi
hinch-off Voltage

balance
long-term

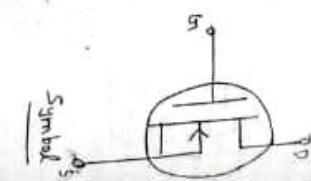• VS = 4V in more forward than so, pinch-off voltage decreases de plateau mode




;

Team or

between
household
household

ion and working of depletion type MOSFET

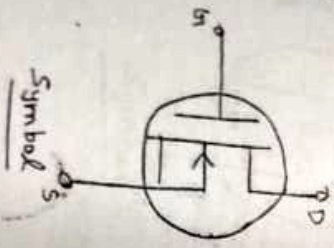depletion type MOSFET has two n regions connected. Drain and source are connected. A n channel is formed which is insulated from n channel (n-FET)



more electrons current increases constant.

This condition is called pinch-off condition. The value of V_{DS} which established this condition is called pinch-off voltage (V_p). After pinch-off current becomes constant.

(ii) $V_{DS} = +V_p$ (> 0), $V_{GS} = -V_p$ (< 0):-

- If V_{GS} is increased then holes in p-type substrate move towards the channel.
- So, recombination process occurs in channel.
- So, pinch-off condition comes earlier and pinch-off voltage decreases in parabolic manner. This is called depletion mode.


(iii) $V_{DS} = +V_p$ (> 0) and $V_{GS} = -V_p$ (< 0):-

- If positive voltage is applied at gate then electrons in p-type substrate move towards the channel.
- So number of electrons in channel increases. So current I_{DS} increases. This is called enhancement mode.

Characteristics:-


It has two types of characteristics.

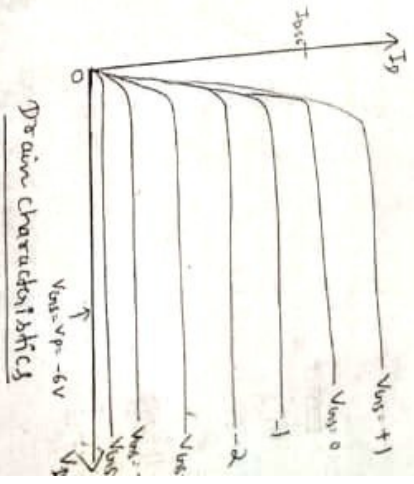i) Drain or output characteristics: It is the curve between drain current (I_D) and drain to source voltage (V_{DS}) at constant gate to source voltage (V_{GS}).



Drain Characteristics

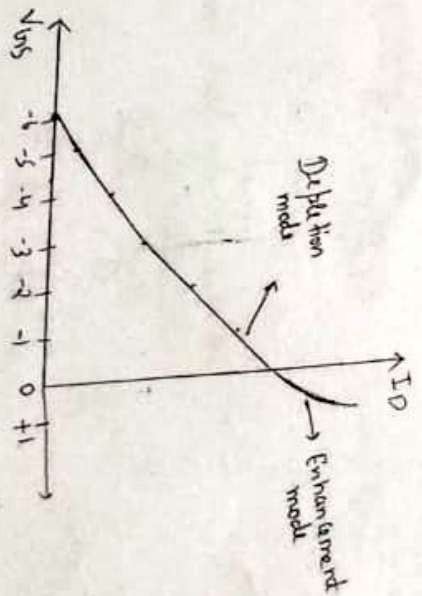(i) Transfer Characteristics: It is the curve between drain current (I_D) and gate to source voltage (V_{GS}) at constant drain to source voltage (V_{DS}).



UNIT-3

* UNIT-3RD *

B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

Q.1) What is an operational amplifier? Draw and explain its characteristics of an ideal op-amp.

Ans. OP-amp is a direct coupled high gain amplifier. It can be used to amplify ac as well as dc signal. It is used for mathematical operation like addition, subtraction, integration, differentiation etc & hence termed as a versatile amplifier. Block diagram of Operational Amplifier.

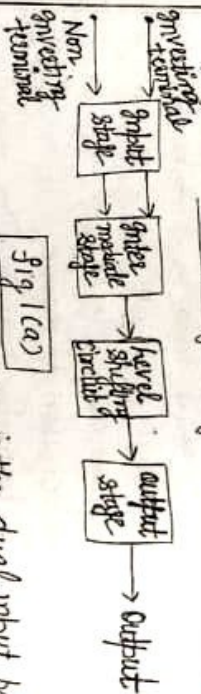


Fig 1(a)

Input stage:- The input stage is the dual input balanced differential amplifier. Its function is to amplify the difference between two input signals. It provides high input impedance, high input impedance.

Intermediate stage:- The overall gain requirement of an op-amp is very high. Intermediate stage is used to provide the required additional gain. It consists of another differential amplifier with dual input and unbalanced (single ended) level shifting circuit. As the OP-amp amplifier consists of also, the small dc voltage level of previous stage is amplified and applied as the input to the next stage. So level shifting circuit is used to bring down the DC level to ground potential.

Output stage:- It is the final stage which is usually consist of a push pull complementary amplifier. The output stage decreases the impedance and increases the current supplying capability of the op-amp.

B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

Q.2) What do you mean by CMRR? It is the ratio of differential mode gain to common mode gain. It is expressed in dB. CMRR = $20 \log \frac{A_d}{A_c}$

Input offset voltage should be $V_{IO} = 0$
Input offset current $I_{IO} = 0$
Input bias current $I_{IB} = 0$

CMRR = $20 \log \frac{A_d}{A_c}$
Vout = $A_d \cdot V_{in}$
Vout = $A_c \cdot V_{in}$

CMRR = $20 \log \frac{A_d}{A_c}$
Vout = $A_d \cdot V_{in}$
Vout = $A_c \cdot V_{in}$


CMRR = $20 \log \frac{A_d}{A_c}$
Vout = $A_d \cdot V_{in}$
Vout = $A_c \cdot V_{in}$

CMRR = $20 \log \frac{A_d}{A_c}$
Vout = $A_d \cdot V_{in}$
Vout = $A_c \cdot V_{in}$

CMRR = $20 \log \frac{A_d}{A_c}$
Vout = $A_d \cdot V_{in}$
Vout = $A_c \cdot V_{in}$

Characteristic of an ideal operational amplifier:-

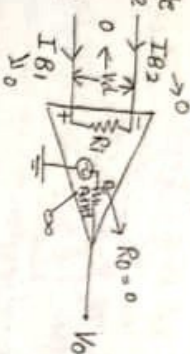- ① Open loop gain should be infinite
- ② Input resistance should be infinite V_i
- ③ Output resistance should be infinite $R_o = \infty$
- ④ Input offset voltage should be zero $V_{IO} = 0$
- ⑤ Input offset current should be zero $I_{IO} = 0$
- ⑥ Output bias current should be zero $I_B = 0$
- ⑦ CMRR should be infinite $CMRR = \infty$



⑧.5 What do you mean by CMRR? determine the output voltage of an op-amp if the input voltage of $V_1 = 150 \mu V$ and $V_2 = 140 \mu V$. The amplifier has differential gain $A_d = 4000$ and $CMRR = 100$.

Ans CMRR :- It is the ability of a op-amp to reject the common mode signal (noise). Sufficiently, CMRR is defined as the ratio of differential mode gain (A_d) and common mode gain (A_c)

for noise (ideal op-amp) $A_c = 0$ So $CMRR = \infty$

for actual op-amp $CMRR = \frac{A_d}{A_c}$ but for practical op-amp it is 90dB.

Numerical:- $CMRR = 100$ where $V_1 = 150 \mu V$ $V_2 = 140 \mu V$

$V_d = V_1 - V_2$ then $V_d = 150 - 140 = 10 \mu V$

$V_c = \frac{V_1 + V_2}{2}$ where $A_d = 4000$ then $100 = \frac{4000}{A_c}$

$CMRR = \frac{A_d}{A_c}$ where $A_d = 4000$ then $100 = \frac{4000}{A_c}$

$V_{out} = A_d V_d + A_c V_c$

$V_{out} = 4000 \times 10 \times 10^{-6} + 40 \times 145 \times 10^{-6}$

$V_{out} = 4 \times 10^{-2} + 580 \times 10^{-5} = (4 + 0.58) \times 10^{-2} = 4.58 \times 10^{-2}$

Q8/ Draw and explain difference & summing amplifier.

Ans Difference or Subtractor amplifier :- A circuit that amplifies the difference between two input signal is called difference amplifier or Subtractor amplifier.

Expression for output voltage:-

Apply KCL at Node B

$\frac{V_a - V_i}{R_1} = \frac{V_i - 0}{R_2}$

$\frac{V_a - V_i}{R_1} = \frac{V_i}{R_2}$

$V_a = V_i \left(\frac{R_2 + R_1}{R_2} \right) \Rightarrow V_a = \left(\frac{R_2 + R_1}{R_2} \right) V_i$ ①

From the concept of Virtual ground

$V_a = 0$

$V_1 - V_2 = 0$

$V_1 = V_2$


But $V_1 = \left(\frac{R_2}{R_1 + R_2} \right) V_a$ [by using eq ①]

So, $V_2 = \left(\frac{R_2}{R_1 + R_2} \right) V_a$ ②

Now, Apply KCL at node A

$\frac{V_3 - V_2}{R_1} = \frac{V_2 - V_o}{R_2}$

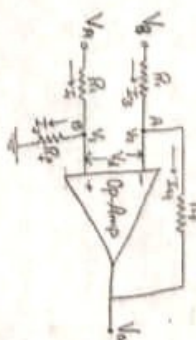$\frac{V_3 - V_2}{R_1} = \frac{V_2 - V_o}{R_2}$



$$V_0 = R_f \left(\frac{R_2 + R_3}{R_1 R_f} \right) V_0 - \frac{R_f}{R_1} V_B$$

$$V_0 = \left(\frac{R_2 + R_3}{R_1} \right) \left(\frac{R_f}{R_2 + R_3} \right) V_A - \frac{R_f}{R_1} V_B \quad [\text{by using eq. 2}]$$

$$V_0 = \frac{R_f}{R_1} V_A - \frac{R_f}{R_1} V_B \Rightarrow V_0 = \frac{R_f}{R_1} (V_A - V_B)$$

So, circuit works as a difference or subtractor amplifier.

If $R = R_f$, $\therefore V_0 = V_A - V_B$

So, circuit works as a difference or subtractor.

Summing Amplifier:- Summing amplifier is an op-amp circuit which can accept two more inputs and produces output as the sum of these inputs.

Expression for op voltage:-

Here, $V_A = 0$ — ①

From Concept of virtual ground

$$V_d = 0$$

$$V_A - V_B = 0$$

$$\therefore V_A = V_B$$

$$\text{But } V_A = 0, \therefore V_B = 0$$

Apply KCL at node A

$$I_1 + I_2 + I_3 = I_4$$

$$\frac{V_1 - V_B}{R_1} + \frac{V_2 - V_B}{R_2} + \frac{V_3 - V_B}{R_3} = \frac{V_B - V_0}{R_f}$$

$$\text{But } V_B = 0, \therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_0}{R_f}$$

$$V_0 = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Case 1st:- If $R_1 = R_2 = R_3 = R$

then, $V_0 = -\frac{R_f}{R} [V_1 + V_2 + V_3]$ So, Circuit works as summing amplifier.

Case 2nd:- If $R_1 = R_2 = R_3 = R_f$

then $V_0 = -[V_1 + V_2 + V_3]$ So, circuit works as a summing amplifier.

Case 3rd:- If $R_1 = R_2 = R_3 = 3R_f$

then $V_0 = -\left[\frac{V_1 + V_2 + V_3}{3} \right]$ So, circuit works as an average amplifier.

Q. Draw the circuit of an integrator and differentiator and explain its working.

Ans/ Integrator:- A circuit that performs the integration of input signal is called integrator circuit.

Expression for output voltage:-

Here, $V_i = 0$ — ①

From Concept of virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$\therefore V_1 = V_2$$

$$\text{But } V_1 = 0$$

$$\text{So } V_2 = 0$$

Apply KCL at node A

$$I_1 = I_2$$

$$\frac{V_i - V_2}{R_1} = C \frac{dV_0}{dt}$$

$$\frac{V_i - V_2}{R_1} = C \frac{d(V_2 - V_0)}{dt}$$

But $V_2 = 0$,

$$\frac{V_i}{R_1} = C \frac{d(-V_0)}{dt}$$

$$\frac{V_i}{R_1} = -C \frac{dV_0}{dt}$$

$$dV_0 = -\frac{1}{R_1 C} V_i dt$$


taking integration on both

$$\int dV_0 = \int -\frac{1}{R_1 C} V_i dt$$

$$V_0 = -\frac{1}{R_1 C} \int V_i dt$$

$$V_0 \propto \int V_i dt$$

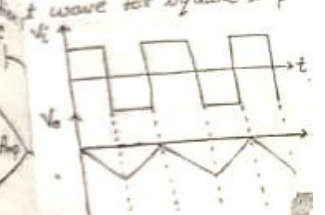output voltage is directly proportional to input voltage. Hence circuit is called integrator.



differentiator:-

used for generating a square wave from a sine wave. It is used in digital to analog converter.

differentiator:- A circuit that produces an output signal which is the derivative of the input signal is called a differentiator circuit.

Here $V_i = 0$ — ①

From Concept of virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$\therefore V_1 = V_2$$

$$\text{but } V_1 = 0$$

$$\text{So } V_2 = 0$$

Apply KCL at Node A

Now taking integration on both side


$$\int dV_o = \int \frac{1}{RC} V_i dt$$

$$V_o = \frac{1}{RC} \int V_i dt$$

$$V_o \propto \int V_i dt$$

Since output voltage is directly proportional to the integration of input signal, hence circuit is called integrator circuit.

Output wave for square input:-

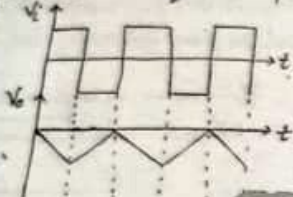

Application:-

- It is used for generating triangular wave.
- It is used in digital to analog converter circuit.
- It is used as low pass filter.

Differentiator:- A circuit that performs the mathematical differentiation of input signal is called differentiator.

Expression for output voltage:-

$$\text{Here } V_i = 0 \quad \text{--- (1)}$$

From concept of virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$\therefore V_1 = V_2$$


$$\text{but } V_1 = 0$$

$$\text{So, } V_2 = 0$$

Apply KCL at Node A,

$$I_1 = I_2$$
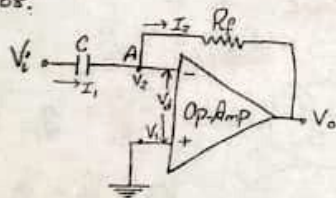
$$C \frac{dV_i}{dt} = \frac{V_2 - V_o}{R_f}$$



$$C \frac{d(V_i - V_2)}{dt} = \frac{V_2 - V_o}{R_f}$$


But $V_2 = 0$,

$$C \frac{dV_i}{dt} = -\frac{V_o}{R_f}$$

$$\Rightarrow V_o = -R_f C \frac{dV_i}{dt} \Rightarrow V_o \propto \frac{dV_i}{dt}$$

Since output voltage is directly proportional to the differentiation of input signal, So, circuit is called differentiator circuit.


Output for triangular input wave:-

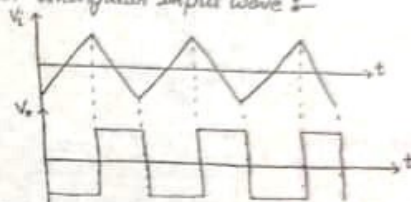

Application:-

- It is used to generate square wave.
- It is also used in analog to digital converter circuit.
- It is used as high pass filter.

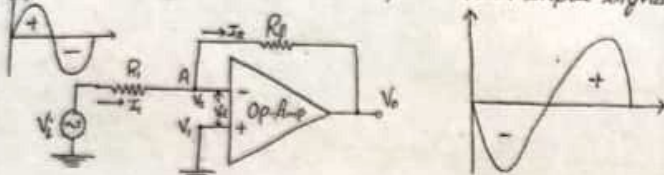Q4/ Explain the working of non inverting & inverting amplifier. Also derive the expression for output voltage.
Ans/ Inverting Amplifier:- An Op-Amp circuit that produce an amplified output signal that is 180° out of phase with input signal.



Expression for Op Voltage:-

Here $V_1 = 0$ — ①

From Concept of Virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$\therefore V_1 = V_2$$

But $V_1 = 0$ [by eq. ①]

So, $V_2 = 0$ — ②

By Applying KCL at Node A

we have, $I_1 = I_2$


$$\frac{V_i - V_2}{R_i} = \frac{V_2 - V_o}{R_f}$$

But $V_2 = 0$, $\therefore \frac{V_i}{R_i} = -\frac{V_o}{R_f}$

$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

- The negative sign denotes a 180° phase difference b/w I/P & O/P.
- Gain can be set to any value by manipulating the value of R_f & R_i .

Non Inverting Amplifier:-

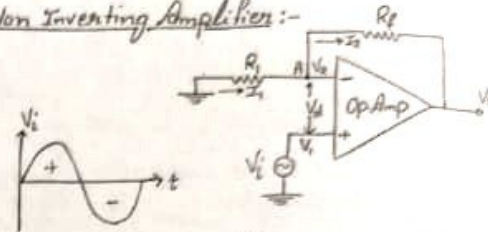

A non-inverting amplifier is an Op-Amp circuit design to provide voltage gain. The input is directly applied to non-inverting input.

Expression for output voltage:-

Here $V_1 = V_i$ — ①

From concept of Virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$\therefore V_1 = V_2$$

But $V_1 = V_i$ [by eq. ①]

So, $V_2 = V_i$ — ②

By applying KCL at Node A

we have, $I_1 = I_2$

$$\frac{0 - V_2}{R_i} = \frac{V_2 - V_o}{R_f}$$

But $V_2 = V_i$, $\therefore -\frac{V_i}{R_i} = \frac{V_i - V_o}{R_f}$

$$\frac{V_o}{R_f} = \frac{V_i}{R_f} + \frac{V_i}{R_i}$$

$$\frac{V_o}{V_i} = \frac{R_f}{R_f} + \frac{R_f}{R_i} \Rightarrow A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

- The positive sign denotes that I/P and O/P are in same phase.
- Gain can be set to any value by manipulating the value of R_f & R_i .

Determine the output of



this is the inverting

$$V_o = -\left[\frac{R_f}{R_i}\right] V_i$$

where $R_f = 330k\Omega$

$$V_1 = V_2 = 0.15V$$


$$V_o = -\left[\frac{330}{33}\right] V_i$$

$$= -\left[\frac{49}{3}\right] V_i$$

$$= -[1.5] V_i$$

$$V_o = -6$$

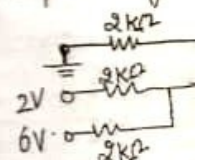explain the concept of the output voltage



Concept of

an ideal op-amp

$$V_d = \frac{V_o}{A_d}$$

$$V_d = 0$$

$$SO V_1 - V_2 = 0$$



Circuit design to provide a non-inverting output

B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]
Determine the output of following circuit. Given $V_1 = V_2 = 0.15V$



that is the inverting scaling Amplifier.


$$V_o = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right]$$

where $R_F = 330k\Omega$ $R_1 = 33k\Omega$ $R_2 = 10k\Omega$
 $V_1 = V_2 = 0.15V$

$$\begin{aligned} V_o &= - \left[\frac{330}{33} \times 0.15 + \frac{330}{10} \times 0.15 \right] \\ &= - \left[\frac{49.5}{33} + \frac{49.5}{10} \right] \\ &= - [1.5 + 4.95] \end{aligned}$$

$$V_o = -6.45V$$

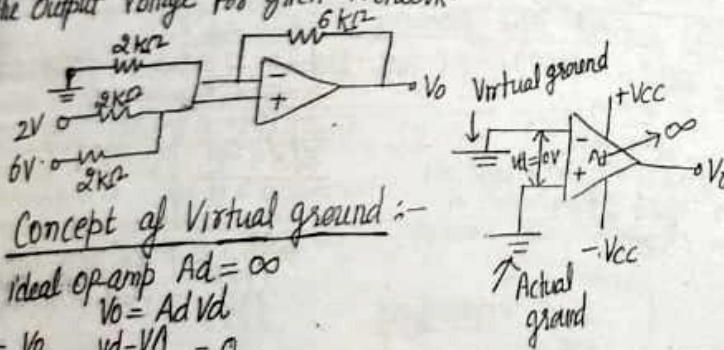Q.7 explain the concept of virtual ground in OP-AMP. Determine the output voltage for given Network.



Ans Concept of Virtual ground :-

For an ideal op-amp $A_d = \infty$
 $V_o = A_d V_d$

$$V_d = \frac{V_o}{A_d} \quad V_d = \frac{V_o}{\infty} = 0$$

$$\text{So } V_1 - V_2 = 0 \text{ then } V_1 = V_2$$


B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

If one terminal of op-amp is connected to ground then other terminal will also be at ground. this is called. Concept of virtual ground. Concept of virtual ground is used to determine closed loop voltage gain and output voltage.

Numerical:- this is non inverting Adder. Hence we have

$$\begin{aligned} V_o &= A_{VF} \times V_i \\ V_o &= \left[1 + \frac{R_F}{R_1} \right] \times \left(\frac{V_a + V_b}{2} \right) \\ V_o &= \left[1 + \frac{6}{2} \right] \times \left[\frac{2+6}{2} \right] \\ &= [1+3] \times [4] = 16 \text{ volts} \\ V_o &= 16 \text{ volts} \end{aligned}$$

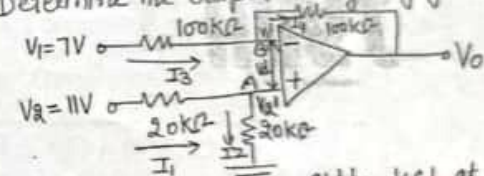Q.8 Determine the output voltage of following circuit.



Sol: Apply KCL at Node A
 $I_1 = I_2$

$$\frac{V_2 - V_2'}{R_1} = \frac{V_2'}{R_2}$$

$$\frac{11 - V_2'}{20} = \frac{V_2'}{20}$$

$$20(11 - V_2') = 20V_2'$$

$$40V_2' = 220$$

$$V_2' = 5.5k\Omega$$

Apply KCL at Node B
 $I_3 = I_4$

$$\frac{V_1 - V_1'}{R_3} = \frac{V_1'}{R_4}$$

where due to virtual ground concept $V_1' = V_2'$

$$\text{then } \frac{7 - 5.5}{100} = \frac{5.5 - V_o}{100}$$

$$1.5 = 5.5 - V_o$$

$$+ V_o = 5.5 - 1.5 = 4$$

$$V_o = 4 \text{ volts}$$

Ans

UNIT-4

B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

UNIT:- 4th

Q1) Convert the following: (1) $(2CCD)_{16} = (?)_8 = (?)_5$

Sol: In Hexadecimal $(1)_{16} \rightarrow 0010110011001101$
 $(1)_8 \rightarrow 026315 \Rightarrow (026315)_8 \rightarrow (?)_5$

Step I:- $(026315)_8 \rightarrow (?)_{10}$

$$\begin{array}{ccccccc} 0 & 2 & 6 & 3 & 1 & 5 \\ \uparrow & \uparrow & \uparrow & \uparrow & \uparrow & \uparrow \\ 8^5 & 8^4 & 8^3 & 8^2 & 8^1 & 8^0 \end{array}$$

$$\rightarrow 0 \times 8^5 + 2 \times 8^4 + 6 \times 8^3 + 3 \times 8^2 + 1 \times 8^1 + 5 \times 8^0$$

$$\rightarrow (11469)_{10}$$

Step II:- $(11469)_{10} \rightarrow (?)_5$

$$\begin{array}{r} 5 \overline{) 11469} \text{ - Remainder} \\ 5 \overline{) 2293} \text{ - 14} \leftarrow \text{LSB} \\ 5 \overline{) 458} \text{ - 5} \\ 5 \overline{) 91} \text{ - 1} \\ 5 \overline{) 18} \text{ - 11} \\ 3 \text{ - 13} \leftarrow \text{MSB} \end{array} = (23114)_{10}$$

Q1(2) Convert $(784)_9 = (?)_{10} = (?)_4$

Sol: Step I:- $(784)_9 = (?)_{10}$

$$\begin{array}{ccc} 7 & 8 & 4 \\ 9^2 & 9^1 & 9^0 \end{array}$$

$$\rightarrow 7 \times 9^2 + 8 \times 9^1 + 4 \times 9^0$$

$$\rightarrow 567 + 72 + 4$$

$$\rightarrow (643)_{10}$$

Step II:- $(643)_{10} = (?)_4$

$$\begin{array}{r} 4 \overline{) 643} \text{ - Remainder} \\ 4 \overline{) 160} \text{ - 13} \leftarrow \text{LSB} \\ 4 \overline{) 40} \text{ - 10} \\ 4 \overline{) 10} \text{ - 10} \\ 2 \text{ - 12} \leftarrow \text{MSB} \end{array} = (22003)_4$$

Q1(3) Convert the following: $(637)_9 = (?)_5$

Sol: Step I:- $(637)_9 \rightarrow (?)_{10}$

$$\begin{array}{ccc} 6 & 3 & 7 \\ 9^2 & 9^1 & 9^0 \end{array}$$

$$\rightarrow 6 \times 9^2 + 3 \times 9^1 + 7 \times 9^0$$

$$\rightarrow 486 + 27 + 7$$

$$\rightarrow (520)_{10}$$

Step II:- $(520)_{10} = (?)_5$

$$\begin{array}{r} 5 \overline{) 520} \text{ - Remainder} \\ 5 \overline{) 104} \text{ - 10} \leftarrow \text{LSB} \\ 5 \overline{) 20} \text{ - 14} \\ 4 \text{ - 10} \leftarrow \text{MSB} \end{array} = (4040)_5$$

B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

Q1) Determine base of the following: $(345)_{10} = (531)_X$

Suppose $(345)_{10} = (531)_X$

$$\begin{array}{ccc} 3 & 4 & 5 \\ \uparrow & \uparrow & \uparrow \\ 10^2 & 10^1 & 10^0 \end{array} = \begin{array}{ccc} 5 & 3 & 1 \\ \uparrow & \uparrow & \uparrow \\ X^2 & X^1 & X^0 \end{array}$$

$$\rightarrow 3 \times 10^2 + 4 \times 10^1 + 5 \times 10^0 = 5 \times X^2$$

$$\rightarrow 300 + 40 + 5 = 5X^2$$

$$\rightarrow 345 = 5X^2 + 3X^1 + 5X^0$$

$$5X^2 + 3X - 344 = 0$$

Suppose we take $X = 8$

$$5(8)^2 + 3(8) - 344 = 0$$

$$5 \times 64 + 24 - 344 = 0$$

$$344 - 344 = 0$$

$$0 = 0$$

Q1(ii) $(2374)_{16} = (9076)_X$

Sol: $2374_{16} = 9076_X$

$$\begin{array}{cccc} 2 & 3 & 7 & 4 \\ 16^3 & 16^2 & 16^1 & 16^0 \end{array} = \begin{array}{cccc} 9 & 0 & 7 & 6 \\ X^3 & X^2 & X^1 & X^0 \end{array}$$

$$2 \times 16^3 + 3 \times 16^2 + 7 \times 16^1 + 4 \times 16^0 = 9 \times X^3$$

$$8192 + 768 + 112 + 4 = 9X^3 + 7X^2 + 6X^1 + 6X^0$$

$$9076 = 9X^3 + 7X^2 + 6X^1 + 6X^0$$

$$9X^3 + 7X^2 - 9070 = 0$$

$$9(10)^3 + 7(10)^2 - 9070 = 0$$

$$9000 + 70 - 9070 = 0$$

then $(2374)_{16} = (9076)_{10}$

Q1(ii) Subtract using 10's complement

Sol: Suppose $A = 9154$ $B = 9636$
 find $A - B = ?$ using 10's complement

Step 1: Find 10's complement of $B = 9636$

10's complement of a number is $10^n - \text{number}$

10's complement of 9636 is $10000 - 9636 = 364$

then add 1 = 365


Now add 9154 with A

$$\begin{array}{r} 9154 \\ + 365 \\ \hline 9519 \end{array}$$

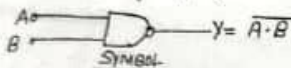Q4-i) what are Universal gates? why are they called so?

Sol: A Universal gate is a gate which can implement any boolean function without need of any other gate. The NAND and NOR are called Universal gates. This is advantageous since NAND and NOR gates are economical and easier to fabricate and are the basic gates used in all IC digital logic families.

NAND Gate:- This is NOT-AND gate. the output of Nand gate is high (1) if any of the input is low. truth table:-



Input	Output Y = A · B
A B	
0 0	1
0 1	1
1 0	1
1 1	0

NOR Gate:-

This is NOT-OR gate. the output of NOR gate is low if any one of the input is high.



truth table:-

Input	Output Y = A + B
A B	
0 0	1
0 1	0
1 0	0
1 1	0

Q4-ii) Draw the logic diagram of EX-OR gate using Universal gate (NAND and NOR)?

Sol: EX-OR using NAND Gate:-


Method 1st:- EX-OR:-

$$Y = \overline{A}B + A\overline{B}$$

$$Y = \overline{A}B + A\overline{B} \quad [\because \overline{A} = A]$$

$$= (\overline{A}B) + (A\overline{B})$$
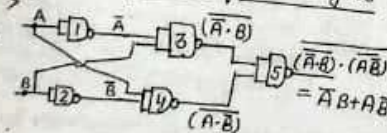
$$= (\overline{A}B) \cdot (\overline{A}B)$$



Method-2nd:- EX-OR:-

$$Y = \overline{A}B + A\overline{B} + A\overline{A}B + A\overline{B}\overline{B}$$


$$= \overline{A}B + A\overline{B} + 0 + 0 \quad [A \cdot \overline{A} = 0 \text{ \& } B \cdot \overline{B} = 0]$$

$$= \overline{A}B + A\overline{B} \quad [\because A \cdot \overline{A} = 0 \text{ \& } B \cdot \overline{B} = 0]$$

$$= \overline{A}(\overline{A}B) + A(\overline{A}B) \quad [\because \overline{A} = A]$$

$$= \overline{A} \cdot (\overline{A}B) + A \cdot (\overline{A}B) \quad [\because \overline{A} = A]$$
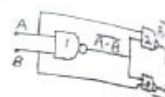
$$= \overline{A} \cdot (\overline{A}B) + A \cdot (\overline{A}B)$$



EX-OR Gate Using NOR Gate:-

Method-1st:- EX-OR:-

$$Y = \overline{A}B + A\overline{B}$$


$$= \overline{A}B + A\overline{B} \quad [\because \overline{A} = A]$$

$$= (\overline{A}B) + (A\overline{B}) \quad [\because \overline{A} = A]$$

$$= (\overline{A}B) \cdot (\overline{A}B) \quad [\because \overline{A} = A]$$

$$= (\overline{A}B) + (A\overline{B}) \quad [\because \overline{A} = A]$$
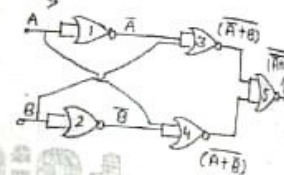
$$= (\overline{A}B) + (A\overline{B}) \quad [\because \overline{A} = A]$$



Method 2ND:- EX-OR:-

$$Y = \overline{A}B + A\overline{B} + A\overline{A}B + A\overline{B}\overline{B}$$

$$= \overline{A}B + A\overline{B} + 0 + 0 \quad [A \cdot \overline{A} = 0 \text{ \& } B \cdot \overline{B} = 0]$$


$$= \overline{A}B + A\overline{B} \quad [\because A \cdot \overline{A} = 0 \text{ \& } B \cdot \overline{B} = 0]$$

$$= \overline{A}(\overline{A}B) + A(\overline{A}B) \quad [\because \overline{A} = A]$$

$$= \overline{A} \cdot (\overline{A}B) + A \cdot (\overline{A}B) \quad [\because \overline{A} = A]$$

$$= \overline{A} \cdot (\overline{A}B) + A \cdot (\overline{A}B) \quad [\because \overline{A} = A]$$
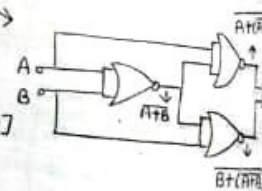
$$= \overline{A} \cdot (\overline{A}B) + A \cdot (\overline{A}B) \quad [\because \overline{A} = A]$$



what are MAXTERM and MINTERM?

Y(A, B, C, D) = (A + B + C + D)

MAX TERM:- Each term in the sum of products is called a max term. It is represented by a max term uncomplemented variable is 1. Complemented variable is 0.

MIN TERM:- Each term in the sum of products is called a min term. It is represented by a min term uncomplemented variable is 1. Complemented variable is 0.

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)




Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

Y(A, B, C, D) = (A + B + C + D)

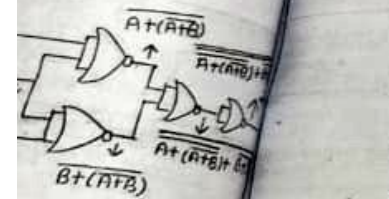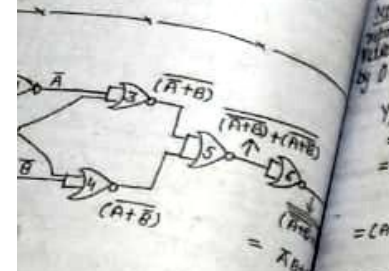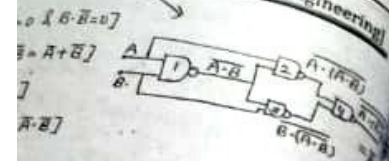

B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

Q.5 What are MAXTERM and MINTERM? Convert the following into POS Format:

$Y(A, B, C, D) = (A + B + C) \cdot (A + D)$
 MAX TERM: Each term in standard or canonical POS (Product of Sums) is called max term. It is represented by m . max term is opposite of minterm. max term uncomplemented variable is represented by 0 (i.e. $A=0$) and complemented variable is represented by 1 (i.e. $\bar{A}=1$)

MIN TERM: Each term in standard or canonical SOP is called min term. It is represented by m . min term is opposite of max term. In min term uncomplemented variable is represented by 1 (i.e. $A=1$) and complemented variable is represented by 0 (i.e. $\bar{A}=0$)

$$Y = (A + B + C) \cdot (A + D)$$

$$= (A + B + C + D \bar{D}) \cdot (A + B \bar{B} + C \bar{C} + D)$$

$$= (A + B + C + D) \cdot (A + B + C + \bar{D}) \cdot (A + B + C + D) \cdot (A + B + C + \bar{D})$$

$$= (A + B + C + D) \cdot (A + B + C + \bar{D}) \cdot (A + B + C + D) \cdot (A + B + C + \bar{D})$$

$$= (A + B + C + D) \cdot (A + B + C + \bar{D}) \cdot (A + B + C + D) \cdot (A + B + C + \bar{D})$$

Q.6 Minimize the following using K-MAP technique:-

$$F(A, B, C, D) = A \bar{B} \bar{C} + A \bar{B} C + A \bar{B} C \bar{D} + A \bar{B} C D + d(1, 5)$$

As we know this is SOP condition so $\bar{A}=0$ & $A=1$ these are minterms.

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00		X		
$\bar{A}\bar{B}$ 01		X		
$\bar{A}\bar{B}$ 11				
$\bar{A}\bar{B}$ 10				

$$F(A, B, C, D) = A \bar{B} \bar{C} + B C D + \bar{A} B C + \bar{A} D$$


B. Tech I Year [Subject Name: Fundamentals of Electronics Engineering]

Q.7 Simplify the following function using K-map:
 $F(A, B, C, D) = \sum(1, 3, 4, 5, 6, 7, 9, 11, 13, 15)$ Also implement the simplified function using basic gates only

Sol: this is SOP condition. So these are minterms. Here $\bar{A}=0$ & $A=1$

Implementation using Basic gates

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00				
$\bar{A}\bar{B}$ 01				
$\bar{A}\bar{B}$ 11				
$\bar{A}\bar{B}$ 10				

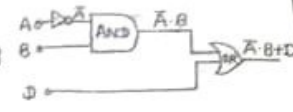

$$F(A, B, C, D) = \bar{A} \cdot B + D$$


Q.8 Minimize using K-map and realize using NOR gates only.

$$F(A, B, C, D) = \sum(3, 4, 5, 7, 9, 13, 14, 15) \cdot d(0, 2, 8)$$

Sol: this is POS condition. So these are maxterm. then $A=0$ & $\bar{A}=1$

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00	X			
$\bar{A}\bar{B}$ 01				
$\bar{A}\bar{B}$ 11				
$\bar{A}\bar{B}$ 10				
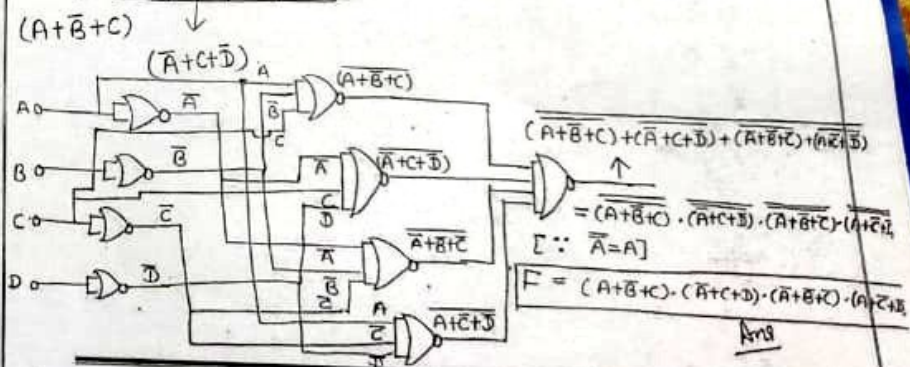
$$F = (A + \bar{B} + C) \cdot (\bar{A} + C + D) \cdot (\bar{A} + B + \bar{C}) \cdot (A + \bar{C} + \bar{D})$$



Ans

UNIT-5

UNIT-5

Q1) Draw and explain the block diagram of a communication system. (Or) Explain the elements of a communication system with the help of block diagram.

Ans → Communication is the transfer of info from point A to point B using electricity or radio. Communication can be divided into three parts: (i) Transmitter (ii) channel (iii) Receiver.

(i) Transmitter: The Transmitter section contains the following blocks:

(A) Information source: It is used to generate a message signal which may be in the form of audio, video or data.

(B) Transducer: - It is a device which converts one form of energy into another. Here it converts a message signal into an electrical signal.

(C) Modulator - Here a low-frequency message signal is superimposed on a high-frequency carrier signal so that it can cover a long distance.

(D) Amplifier - This block is used to enhance the strength of the signal before transmission.

(E) Transmitting Antenna: It is used to convert an electrical signal into an electromagnetic wave, which can travel in the atmosphere.

(ii) Channel: - The EM waves radiated from the transmitting antenna travel through a path or medium to reach the receiver. This path or medium is called a channel.

There are two types of channels: (i) Wired channel: i.e. optical fibre (ii) Wireless channel

(i) Noise: It is an unwanted signal that is present with the transmitted signal. There are two types of noise: (i) natural noise (ii) man-made noise. Examples of man-made noise are automobiles, radios, etc.

(ii) Receiver: The receiver section contains the following blocks: (A) Receiving Antenna: It receives the electromagnetic wave from the transmitter and converts it into an electrical signal.

(B) Amplifier: This block is used to enhance the strength of the received signal.

(C) Demodulator: It is used to extract the message signal from the modulated signal.

(D) Transducer: It is used to convert the message signal into a form that can be understood by the receiver.

There are two types of Channel.
Wired Channel: Here the medium is physical like optical fibre, coaxial cable etc.
Wireless Channel: Here medium is air.

Noise: It is unwanted signal which will mix with the transmitted signal when it is in channel. There are two types of noise.

Natural noise: The source of natural noise is radiation from sun and stars.
Man made noise: The source of man made noise are automobiles, motors etc.


Receiver: This section consist of.

1) Receiving Antenna: It is used to convert received em waves from the channel into electrical signal.

2) Amplifier: The signal received at the receiver has suffered various types of losses in the atmosphere. An amplifier is needed to increase its strength.


3) Demodulator: It is used to separate carrier from the message signal.

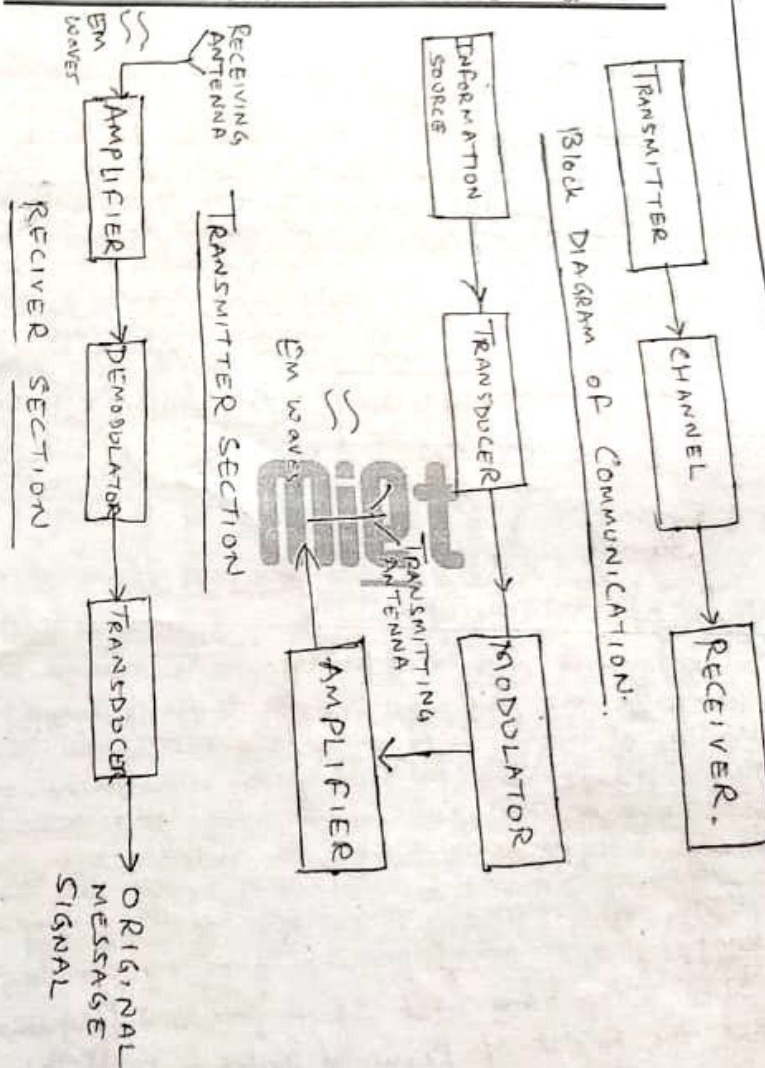4) Transducer: Finally this circuit is used to convert received message signal in the electrical form to original form (it may be text, audio, data).



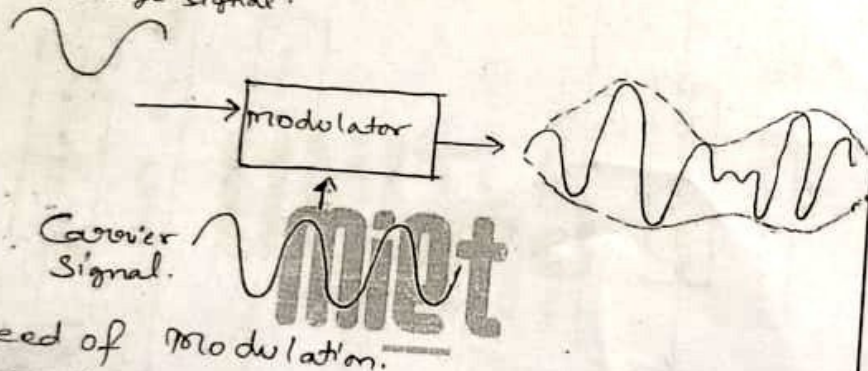Q.1) What is Modulation? Why modulation is required in Communication System?

Ans MODULATION $\rightarrow$ It is a process in which low frequency message signal is superimposed on the high frequency carrier wave. In this process one of the parameters of the carrier varies according to message signal.



Need of Modulation.

- Interference or mixing Problem $\rightarrow$ As message signals are generally low frequency signals there is large probability of mixing with other signals of the same frequency range also present in the atmosphere. So low frequency message signals are sent through high frequency carrier wave to avoid such problems.
- Height of Antenna $\rightarrow$ Practical height of transmitting or receiving antenna $= \frac{\lambda}{4}$, where λ is the wavelength of the signal being used. If we use low frequency signal, the height of required antenna is of the order of kilometers.

Q.2) The antenna current of an AM transmitter is 8A when only the carrier is sent, but it increases to 8.93A when the carrier is modulated by a single sine wave. Find Percentage modulation. Determine antenna current when the Percent of modulation is 0.8.

Sol: We know that

$$I_t = I_c \sqrt{1 + \frac{m^2}{2}} \quad \text{--- (A)}$$

where transmitting current of Antenna $I_t = 8.93A$

Carrier current $I_c = 8A$

put the values of I_t & I_c in eq (A) then we get

$$I_t = I_c \sqrt{1 + \frac{m^2}{2}}$$

$$\frac{I_t}{I_c} = \sqrt{1 + \frac{m^2}{2}}$$

taking square both side then $\left(\frac{I_t}{I_c}\right)^2 = \left(\sqrt{1 + \frac{m^2}{2}}\right)^2$

$$\frac{I_t^2}{I_c^2} = 1 + \frac{m^2}{2} \Rightarrow \frac{(8.93)^2}{(8)^2} = 1 + \frac{m^2}{2}$$

$$\frac{79.7449}{64} = 1 + \frac{m^2}{2}$$

$$1.2460 = 1 + \frac{m^2}{2}$$

$$\frac{m^2}{2} = 0.2460$$

$$m^2 = 0.4920$$

$$m = \sqrt{0.4920}$$

$$m = 0.7014$$

$$\therefore \text{Modulation} = m \times 100 = 0.7014 \times 100 = 70.14\%$$

$$\therefore m = 70.14\%$$

What is amplitude Modulation? Derive its expression. Also draw its frequency Spectrum. Explain with the help of proper waveform. Derive the expression for the total power radiated by modulated signal. Also calculate modulation efficiency.

Amplitude Modulation:- In amplitude Modulation, the amplitude of the Carrier Signal is modulated according to the instantaneous amplitude of the message signal. In this process frequency and phase of the Carrier remains constant.

Expression of Amplitude Modulated (AM) Signal.

$$m(t) = V_m \cos(2\pi f_m t)$$

$$c(t) = V_c \cos(2\pi f_c t)$$

$$s_{AM}(t) = [V_c + m(t)] \cos 2\pi f_c t$$

$$= [V_c + V_m \cos(2\pi f_m t)] \cos 2\pi f_c t$$

$$m = \frac{V_m}{V_c}$$

m is modulation Index

$$\Rightarrow V_c \cos 2\pi f_c t + V_m \cos 2\pi f_m t \cos 2\pi f_c t$$

$$\Rightarrow V_c \cos 2\pi f_c t + \frac{V_m}{2} [\cos 2\pi (f_c + f_m) t + \cos 2\pi (f_c - f_m) t]$$

$$\Rightarrow V_c \cos 2\pi f_c t + \frac{V_m}{2} \frac{V_c}{V_c} \cos 2\pi (f_c + f_m) t + \frac{V_m}{2} \frac{V_c}{V_c} \cos 2\pi (f_c - f_m) t$$

$$\Rightarrow V_c \cos 2\pi f_c t + m \frac{V_c}{2} \cos 2\pi (f_c + f_m) t + m \frac{V_c}{2} \cos 2\pi (f_c - f_m) t$$

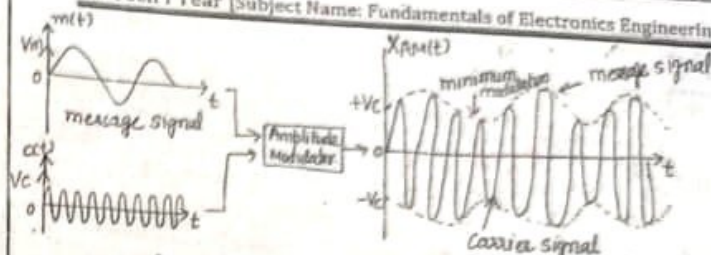
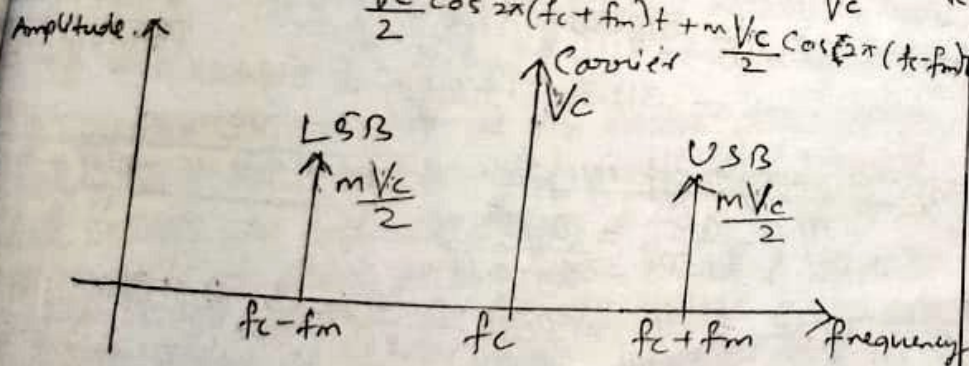


Fig 1 For Amplitude Modulation / (Waveform)

* Expression for total power radiated by the modulated signal & efficiency:- AM wave has three components. Unmodulated carrier, lower sideband & upper side band.

therefore $P_{Total} = P_c + P_{USB} + P_{LSB}$

$$= \frac{V_{Carrier}^2}{R} + \frac{V_{USB}^2}{R} + \frac{V_{LSB}^2}{R}$$

① Carrier Power P_c :-

$$P_c = \frac{V_c^2}{R} \rightarrow \text{carrier power}$$

$$\therefore \text{the average carrier power} = \frac{(V_c / \sqrt{2})^2}{R} = \frac{V_c^2}{2R}$$

② Power in side band:- $P_{USB} = P_{LSB} = \left(\frac{mV_c}{2\sqrt{2}}\right)^2 = \frac{m^2 V_c^2}{8R} = \frac{m^2 P_c}{4}$

③ Total Power P_t :- $P_t = P_c + P_{USB} + P_{LSB}$

$$P_t = P_c + \frac{m^2 P_c}{4} + \frac{m^2 P_c}{4} = P_c \left(1 + \frac{m^2}{2}\right)$$

④ Transmission Efficiency:- η :- It is the ratio of the Transmitted power which contains the information (i.e. sum of lower side band power and upper side band power) to the total Transmitted power P_t .

$$\text{Transmission efficiency:- } \eta = \frac{P_{LSB} + P_{USB}}{P_t} = \frac{\left[\frac{m^2 P_c}{4} + \frac{m^2 P_c}{4}\right]}{P_c \left[1 + \frac{m^2}{2}\right]} = \frac{\frac{m^2}{2}}{1 + \frac{m^2}{2}}$$

$$\eta = \frac{m^2}{2 + m^2}$$

$$\therefore \eta = \frac{m^2}{2 + m^2} \times 100\%$$

Q3-ii) An AM radio transmitter radiates 6 kw power when modulation % is 70%. Determine the carrier power.

Ans For AM signal, power relation is

$$P_t = P_c \left(1 + \frac{m^2}{2}\right)$$

Here $P_t = 6 \text{ kw}$, $m = 0.70$

$$\text{So, } P_c = \frac{P_t}{1 + \frac{m^2}{2}} = \frac{6 \times 10^3}{1 + \frac{0.49}{2}} = 4.82 \text{ kw}$$

Q4) An audio frequency signal $5 \sin 2\pi \times 500t$ is used to amplitude modulate a carrier of $25 \sin 2\pi \times 10^5 t$. Calculate (i) Modulation Index (ii) Side band frequency (iii) Amplitude of each side band (iv) Bandwidth required (v) Total Power (vi) Transmission Efficiency.

Ans Given: $m(t) = 5 \sin 2\pi \times 500t$
 $c(t) = 25 \sin 2\pi \times 10^5 t$

(i) Modulation index, $m = \frac{A_m}{A_c} = \frac{5}{25} = 0.2 \text{ Ans}$

(ii) Side band frequency. $f_c + f_m$ & $f_c - f_m$

Here $f_c = 10^5 \text{ Hz} = 100 \text{ kHz}$
& $f_m = 500 \text{ Hz} = 0.5 \text{ kHz}$

So $f_c + f_m = 100 + 0.5 = 100.5 \text{ kHz}$
& $f_c - f_m = 100 - 0.5 = 99.5 \text{ kHz}$ } Ans.

(iii) Amplitude of side bands = $\frac{m \cdot A_c}{2}$ Or $\frac{m \cdot V_c}{2}$

$$= \frac{0.2 \times 25}{2} = 2.5 \text{ V Ans.}$$

(iv) Band width = $2f_m = 2 \times 500 \text{ Hz} = 1 \text{ kHz Ans}$

(v) Total Power $P_t = P_c \left(1 + \frac{m^2}{2}\right)$
where $P_c = \text{carrier power}$

$$P_c = \frac{V_c^2}{2R} \text{ where } R = 1 \Omega \quad V_c = 25$$

$$\text{then } P_c = \frac{(25)^2}{2 \times 1} = \frac{625}{2} = 312.50 \text{ Watt}$$

$$P_t = P_c \left(1 + \frac{m^2}{2}\right) = 312.50 \left(1 + \frac{0.2^2}{2}\right) = 312.50 \left(1 + \frac{0.04}{2}\right) = 312.50 \times 1.02 = 318.7500$$

$$P_t = 318.75 \text{ Watt}$$

(vi) Transmission efficiency:-

$$\eta = \frac{m^2}{2 + m^2} = \frac{0.2^2}{2 + 0.2^2}$$

$$\eta = \frac{0.04}{2 + 0.04} = \frac{0.04}{2.04} = \frac{4}{204} = \frac{1}{51} = 0.0196$$

$$\therefore \eta = 0.0196 \times 100 = 1.96\% \text{ Ans}$$

Describe AM modulation & Demodulation techniques with diagram

Amplitude Modulation:-

AM signal can be generated with the help of square law modulator circuit as shown:-

modulator circuit consist of a non-linear device

A bandpass filter

Carrier source and modulating signal.

$$V_1(t) = m(t) + V_c \sin \omega_c t \quad \text{--- (1)}$$

$$V_2(t) = a V_1(t) + b V_1^2(t) \quad \text{--- (2)}$$

put (1) in eq. (2)

$$V_2(t) = a[m(t) + V_c \sin \omega_c t] + b[m^2(t) + V_c^2 \sin^2 \omega_c t + 2V_c m(t) \sin \omega_c t]$$


In these term only 2nd & 4th term are useful. Here LC tuned circuit is used acting as bandpass filter. It frequency response.

$$V_o(t) = a V_c \sin \omega_c t + 2b V_c m(t) \sin \omega_c t$$

$$V_o(t) = [a V_c + 2b m(t)] \sin \omega_c t$$

square law modulator can be used to generate AM signal. BW = 2 fm

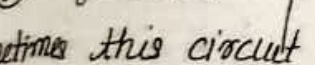
Amplitude demodulator:- linear diode detector or envelope detector can be used for detection of AM signal.



Here diode is working as main detecting component.

So sometimes this circuit is also called diode detector.

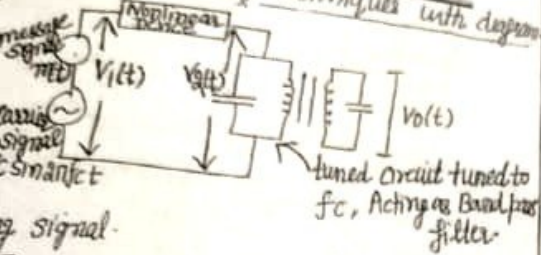During positive cycle of the input (modulated) signal diode conducts and capacitor charges to its peak value. During negative cycle, the diode gets reverse biased & capacitor discharge through resistor R. So the o/p voltage across capacitor is a spiky envelope of the AM wave, which is same as the message signal.



Q6. Describe briefly Satellite Communication?

Define the terms of satellite communication.

Answer A satellite is a smaller object that revolves around a larger object in space. For example, moon is a natural satellite of earth. When communication takes place between two earth stations through a satellite, then it is called as satellite communication. In this communication, E.M. waves are used as carrier signals. These signals carry the information such as voice, audio, video or any other data between ground and space and vice versa.

There are two types of satellite

- i) Artificial
- ii) Natural

a) Artificial Satellite → Artificial satellites are specially designed and launched into space for different applications such as:- weather monitoring, navigation, T.V, Mobile communication, planetary research etc.

Ex → INSAT, IRS, GSAT etc.

b) A natural Satellite → Natural satellite is any celestial body in space that orbits around a large body. Earth revolves around sun, so it is a satellite. Similarly moon revolves around earth, so it is also a natural satellite.


Application of satellite communication:- ① telephone, television, Digital cinema, Radio broadcasting, Internet access, Military, Disaster management, Amateur radio.

Need of Satellite Communication :-

In communication process, transmission of signals used to occur in two different ways in earlier days. These are - ground wave propagation and sky wave propagation. But maximum distance of communication is limited to 1500km in both propagations. Satellite communication overcomes this limitation. Here communication beyond line of sight distance is possible.

Working → Satellite communication involves four steps:-

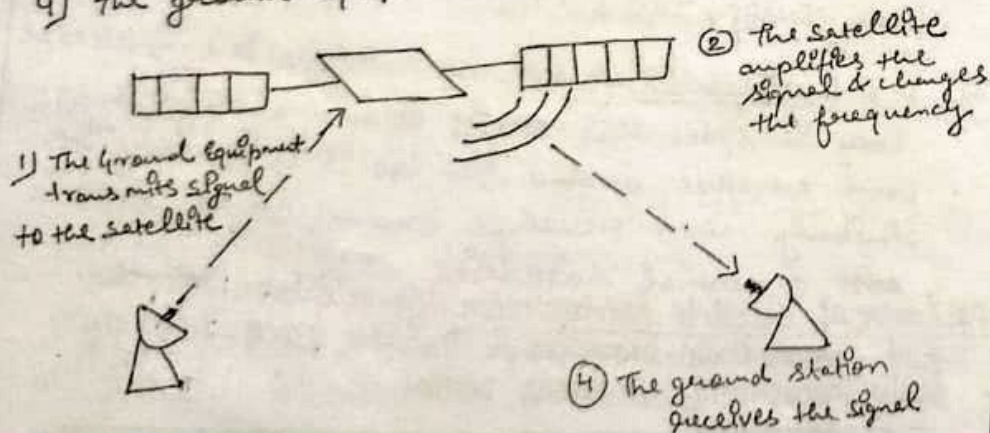- 1) An Uplink earth station or other ground equipment transmits the desired signal to the satellite. The frequency with which the signal is transmitted is called Uplink frequency.
- 2) The satellite amplifies the incoming and changes the frequency.
- 3) The satellite transmits the signal back to Earth. The freq. of the signal is transmitted is called Downlink freq.
- 4) The ground equipment receives the signal.



Q7(i) What is RADAR? Write down two applications of RADAR.

Ans Radar is a detection system that uses radio waves to determine the range angle velocity of the objects. It can be used to detect aircraft, ships, spacecraft, guided missiles etc.

Elements of Radar Communication System

- ① Transmitter
- ② Antenna
- ③ Receiver
- ④ Power supply.

Radio wave from the transmitter, reflects off the object & return to the receiver, giving information about the object's location and speed.


down two applications

that uses range angle and used to detect missiles

ation system

er, reflect
er, giving

Transmitter of radar system emits waves in predetermined direction. When these signals meet an object, they are usually reflected in many directions. The signals reflected towards the Radar receiver are used for deflection purpose. The time taken by the signal to reach the destination & come back to the radar receiver is used for obtaining the range of the object to be detected. If the object is not fixed & moving away or towards the transmitter, there will be slight change in the frequency of received signal due to Doppler effect.

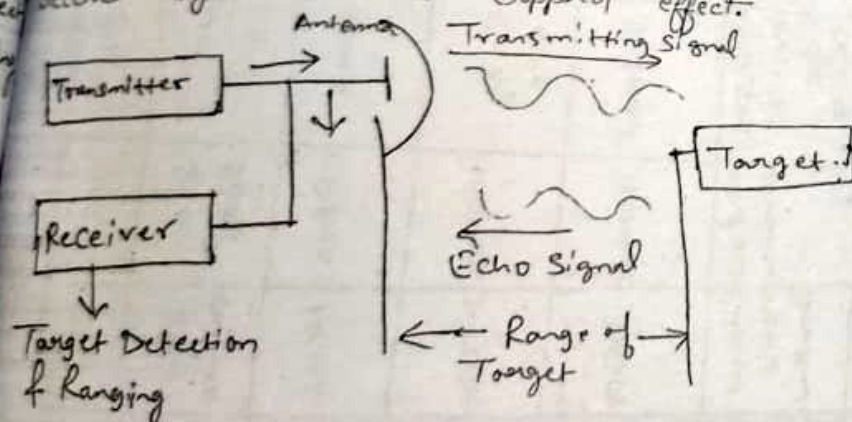

RADAR Application :- ① In Military Applications ② Air traffic Control ③ Remote Sensing ④ Ground traffic Control ⑤ Space.

Q.7⑩ Write short Notes on Wireless Communication.

Wireless Communication:- Wireless communication is the transmission of voice and data without cable or wires. In place of a physical connection, data travels through electromagnetic signal broadcast from sending facilities to intermediate and end user devices.

The first wireless communication went on the air in the early 20th century using radiotelegraphy, which is radio communication using Morse Code or other coded signal. Later as Modulation made it possible to transmit voice and music wirelessly, the medium became known as radio. Wireless transmitters use electromagnetic waves to carry voice, data, video, or signals over a communication path. Some examples of wireless devices are, cellular phone, cordless telephones, GPS, cordless computer system, Wireless LAN, Wireless Routers.

Q.8 Explain different generations and standards in cellular communication. :-

Sol: Evolution of Mobile communication:- Mobile Wireless communication system has gone through several evolution stages in the past few decades after the introduction of first generation. Mobile network in early 1980s. Due to huge demand for more connection worldwide, mobile communication standard advanced rapidly to support more users.

1G (First Generation Mobile Network):- The first generation of mobile Network was deployed in Japan by Nippon Telephone & Telegraph company in 1979. The system used analog signals & it had many drawbacks due to technology limitations.

2G (Second Generation):- this generation saw the introduction of GSM (Global system for Mobile Communication) technology in the early 90's. It allowed digital voice & data to be sent across the network and allowed users to roam for first time.

2.5G (2.5 Generation):- In the beginning of 2000, an upgradation in technology introduced the packet network which provided high speed data transfer and internet and this generation is called 2.5G. These are used in GPRS, Packet radio, & EDGE.

3G (Third Generation):- It was introduced in 2001. The major aims of third generation mobile network were to facilitate greater voice and data capacity. These are used in video calls, chatting, conferencing, Mobile TV, Video on demand services, navigational maps, Mobile gaming etc.

4G (Fourth Generation):- started in 2010. It is enhanced version of 3G. Network developed by IEEE offers higher data rate and capable to handle more advanced multimedia services. LTE & LTE advanced wireless technology are used in 4G system. Wireless transmission technology like Wimax are used in 4G system to enhance data rate and network performance.

5G (Fifth Generation):- this generation is using advanced technologies to deliver ultra data fast internet and multimedia experience for customers. In order to achieve higher data rate, 5G technology will use millimeter waves and unlicensed spectrum for data transmission. Complex modulation techniques has been developed to support massive data rate.

Q 8 Write short note on evolution of mobile comm from 1G to 5G.

Generation Type	Year	Multiplexing	Bandwidth	Data rate	Application
1G	1980-1990	FDMA	30KHz	24Kbps	Voice (Analog)
2G	1992-2000	TDMA	200KHz	14.4Kbps	Voice & Digital
2.5G	2001-2004	TDMA, CDMA	200KHz	115Kbps	Voice, SMS, MMS
3G	2005-2010	CDMA	5-20 MHz	7.2Mbps	Voice, SMS, MMS + Video calling
4G	2011-2020	OFDMA	100MHz	100Mbps	HD & UHD Streaming, Mobile Broadband
5G	2021 onwards	NOMA	1-2GHz	10Gbps	